

DIGITAL TECHNICS

Dr. Bálint Pődör

*Óbuda University,
Microelectronics and Technology Institute*

3. LECTURE: IMPLEMENTATION OF COMBINATIONAL LOGIC



1st (Autumn) term 2018/2019

3. LECTURE: COMBINATIONAL LOGIC IMPLEMENTATION

1. Implementation of combinational logic, general aspects
2. Multiple output logic networks
3. AND-OR-XOR networks
4. Logic design using functional blocks

SYNTHESIS USING LOGIC GATES

The traditional process of logic synthesis is based on the application of logic gates.

Its more modern variant makes use of programmable logic devices too.

However in many case it is more advantageous to use a logic synthesis procedure based on the application of logic functional blocks.

IMPLEMENTING COMBINATIONAL LOGIC

The different steps involved in the design of a combinational logic circuit are as follows:

1. Statement of the problem.
2. Identification of input and output variables.
3. Expressing the relationship between the input and output variables.
4. Construction of a truth table to meet input–output requirements.
5. Writing Boolean expressions for various output variables in terms of input variables.
6. Minimization of Boolean expressions.
7. Implementation of minimized Boolean expressions.

IMPLEMENTING COMBINATIONAL LOGIC

These different steps are self-explanatory. One or two points, however, are worth mentioning here.


There are various simplification techniques available for minimizing Boolean expressions, which have been discussed in the previously. These include the use of theorems and identities, Karnaugh mapping, the Quine–McCluskey tabulation method and so on. Also, there are various possible minimized forms of Boolean expressions.

The following guidelines should be followed while choosing the preferred form for hardware implementation:

IMPLEMENTING COMBINATIONAL LOGIC

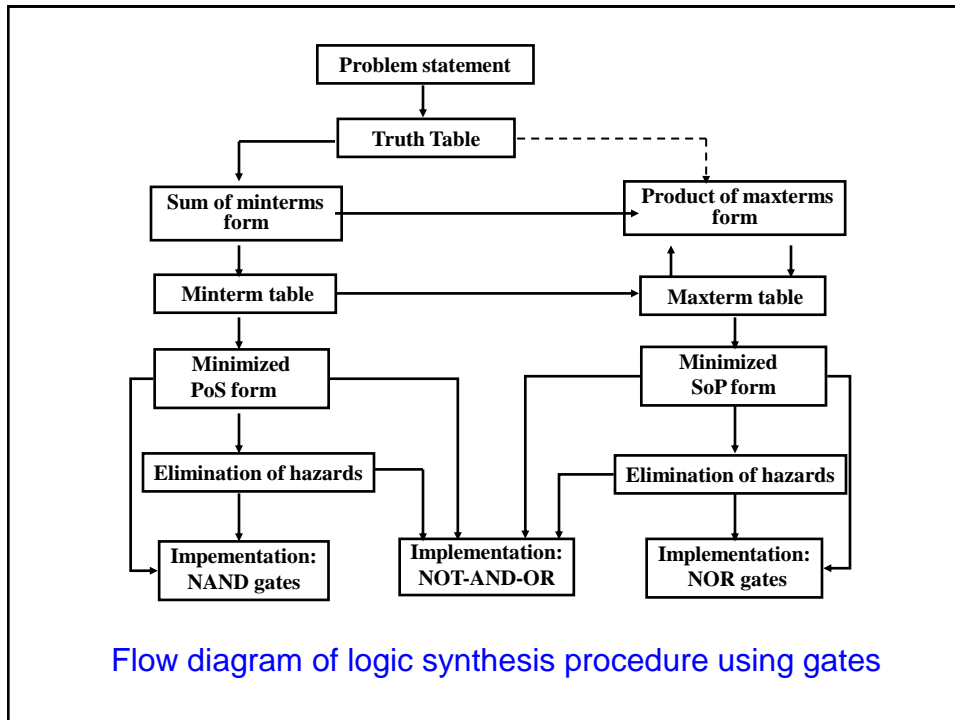1. The implementation should have the minimum number of gates, with the gates used having the minimum number of inputs.
2. There should be a minimum number of interconnections, and the propagation time should be the shortest.
3. Limitation on the driving capability of the gates should not be ignored.

It is difficult to generalize as to what constitutes an acceptable simplified Boolean expression. The importance of each of the above-mentioned aspects is governed by the nature of application.



IMPLEMENTATION OPTIONS

Ready-made catalog-order (modular) devices (gates, functional blocks, etc.)

Custom-design devices


Gate-array devices

Programmable logic devices (PLD), e.g. programmable logic array (PLA), programmable array logic (PAL), etc.

Table look-up (ROM)


Microcomputer

PROGRAMMABLE ARRAY LOGIC

 

16-input, 8-output PAL (P16H8)

PROGRAMMABLE SEQUENTIAL ARRAY

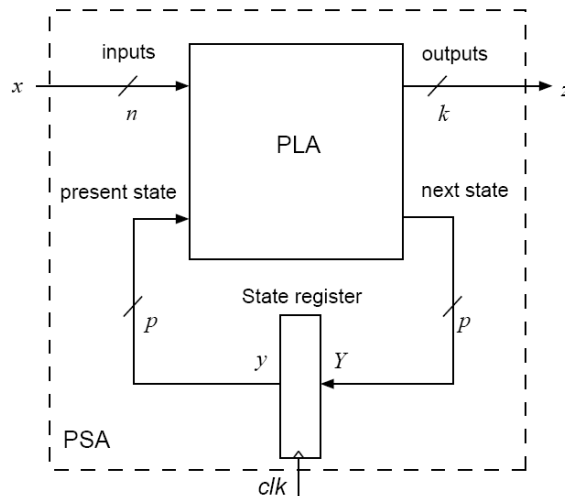

PSA = PLA + registers (flip-flops)

EXAMPLE: CODE CONVERTERS WITH ROM

Various codes are used in digital technics. For the solution of a given task a certain type of code might be the most appropriate, however for an other different task an other code type might be more advantageous.

E. g. in a digital position or angle sensor it is advantageous to use the Gray code. However the treating of measurement data and performing arithmetics would be rather complicated in Gray code, for this the binary code is the best choice.

The various BCD type codes play an important role in the information exchange between the digital systems and human beings, however inside the system itself the use of such code is disadvantageous because of memory capacity usage, and more complicated arithmetics.

For this reason code conversion is a commonly occurring task in various digital systems.

11

ROM APPLICATIONS: CODE CONVERSIONS

One important application of ROMs in combinational logic is the code conversion.

n-bit code \rightarrow m-bit code \rightarrow necessary memory capacity:
 $m \times 2^n$.

Practical examples:


8-bit binary code \rightarrow 8-bit Gray code: 256x8 ROM.

13-bit binary code \rightarrow 4 tetrad BCD code:

Two 8-kbyte capacity EPROM, 1s, and 10s, and 100s and 1000s respectively, (13 bit: 0-8191).

12


CODE CONVERSION USING ROM

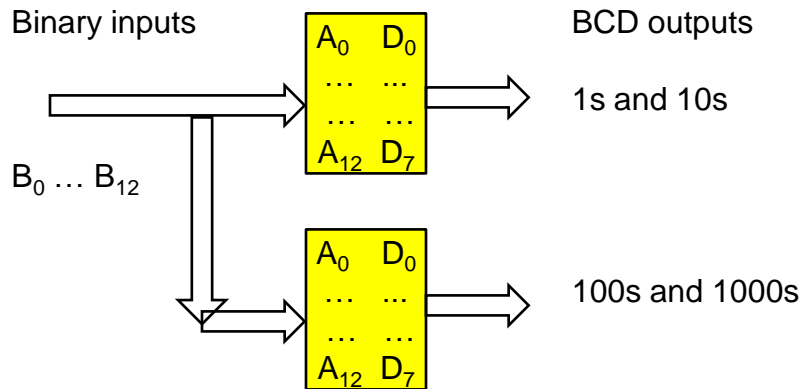

13-bit binary code to 4 tetrad BCD code converter

ROM BASED LOGIC: MULTIPLIER


	X	Y	Z
0*0	00	00	0000
0*1	00	01	0000
0*2	00	10	0000
0*3	00	11	0000
1*1	01	01	0001
1*2	01	10	0010
1*3	01	11	0011
2*0	10	00	0000
2*1	10	01	0010
2*2	10	10	0100
2*3	10	11	0110
3*0	11	00	0000
3*1	11	01	0011
3*2	11	10	0110
3*3	11	11	1001

 

Fast, simple, cheap,
Can generate any function
(look-up-table, LUT)


LUT based logic is used in
several types of FPGAs.

8x8 BIT COMBINATIONAL MULTIPLIER

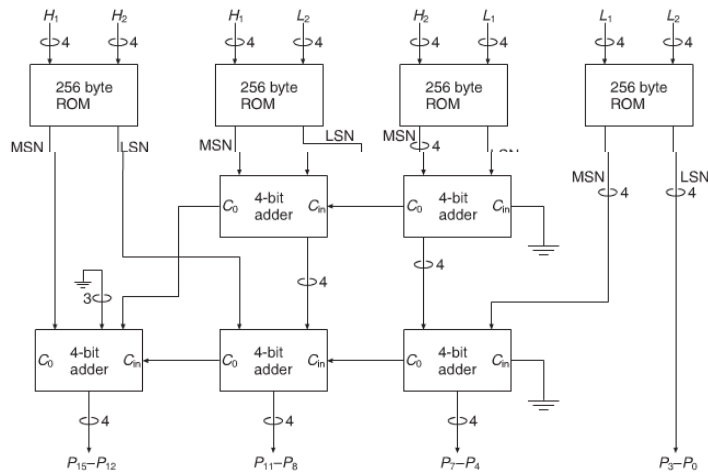


4x4 bit partial products are generated by four 256x8 bit ROMs

LUT(ROM) BASED SYSTEM LOGIC BLOCK

 

In general, a logic block (CLB or LAB) consists of a few logical cells (called ALM, LE, Slice etc). A typical cell consists of a 4-input Lookup table (LUT), a Full adder (FA) and a D-type flip-flop. The LUT are in this figure split into two 3-input LUTs. In *normal mode* those are combined into a 4-input LUT through the left mux.

 MINIMIZATION AND IMPLEMENTATION OF MULTIPLE OUTPUT NETWORKS: PRINCIPLE AND DEMO EXAMPLE



$$F_a = \Sigma^4(5,12,13)$$


$$F_b = \Sigma^4(3,5,7)$$

B "Elementary" implementation:
four 3-input AND gates and
two 2-input OR gates

Cost function (pin count):
 $4 \times 3 + 2 \times 2 = 16$
Gate count: 6

17

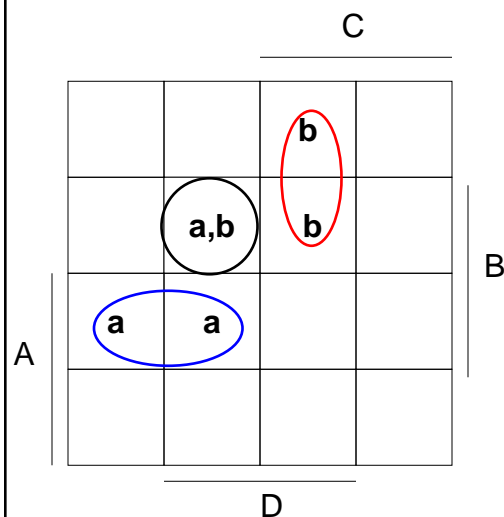MINIMIZATION AN IMPLEMENTATION OF MULTIPLE OUTPUT NETWORKS




$$F_a = \Sigma^4(5,12,13)$$

$$F_b = \Sigma^4(3,5,7)$$

18

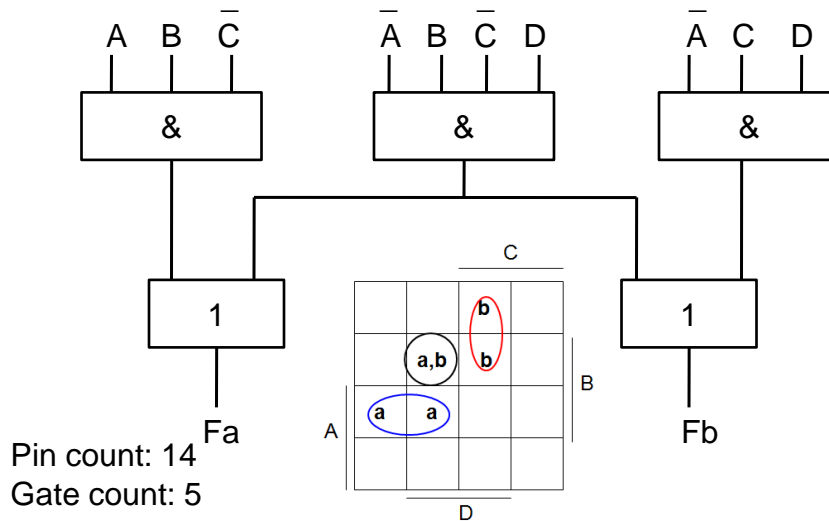MINIMIZATION AN IMPLEMENTATION OF MULTIPLE OUTPUT NETWORKS



MINIMIZATION AN IMPLEMENTATION OF MULTIPLE OUTPUT NETWORKS

In this example the independent minimization of the two outputs of the pin count is 16, the common minimization yields 14 pins. The gate counts were 6 and 5 respectively.

The common minimization is generally noticeably optimal, in this case the pin number decreased by 12.5 percent.

The common implicant can be found by graphical or by numerical methods. For more than 3 or for outputs the transparency of the graphical method is strongly reduced, in such cases e.g. the appropriately modified Quine-McCluskey algorithm can be used.

EXAMPLE: MINIMIZATION OF THREE OUTPUT LOGIC FUNCTION

Determine the simplest conceptual two-level AND-OR logic diagram of the three output logic network:

$$F_a = \Sigma^4(0,1,5,6,7,13)$$

$$F_b = \Sigma^4(0,1,5,10-15)$$

$$F_c = \Sigma^4(0,1,8-11,14,15)$$

The common prime implicants of F_a and F_b are the prime implicants of the product function $F_{ab} = F_a F_b$, etc.

21

COMMON (PRIME) IMPLICANTS

Product functions (pairs):

$$F_a = \Sigma^4(0,1,5,6,7,13)$$

$$F_b = \Sigma^4(0,1,5,10-15)$$

$$F_c = \Sigma^4(0,1,8-11,14,15)$$


$$F_{ab} = F_a F_b = \Sigma^4(0,1,5,13) = m(0,1) + m(5,13)$$

$$F_{bc} = F_b F_c = \Sigma^4(0,1,10,11,14,15) = (0,1) + m(10,11,14,15)$$

$$F_{ca} = F_c F_a = \Sigma^4(0,1) = m(0,1)$$

22

RESULT OF MINIMIZATION (1)

 



Principle: the common prime implicants occurring in more outputs are implemented only once.

Fa, Fb, Fc: $/A/B/C$ $m(0,1)$
 Fa, Fb: $B/C D$ $m(5,13)$
 Fa, Fb: $A C$ $m(10,11,14,15)$

23

ANOTHER EXAMPLE: BCD TO 7-SEGMENT DISPLAY CONTROLLER

  - Understanding the problem
 - Input is a 4 bit BCD digit (A, B, C, D)
 - Output is the control signals for the display (7 outputs C0 – C6)
- Block diagram




24

FORMALIZE THE PROBLEM

- Truth table
 - Show don't cares
- Choose implementation target
 - If ROM, we are done
 - Don't cares imply PAL/PLA may be attractive
- Follow implementation procedure
 - Minimization using K-maps

A	B	C	D	C0	C1	C2	C3	C4	C5	C6
0	0	0	0	1	1	1	1	1	1	0
0	0	0	1	0	1	1	0	0	0	0
0	0	1	0	1	1	0	1	1	0	1
0	0	1	1	1	1	1	1	0	0	1
0	1	0	0	0	1	1	0	0	1	1
0	1	0	1	1	0	1	1	0	1	1
0	1	1	0	1	0	1	1	1	1	1
0	1	1	1	1	1	1	0	0	0	0
1	0	0	0	1	1	1	1	1	1	1
1	0	0	1	1	1	1	0	0	1	1
1	0	1	-	-	-	-	-	-	-	-
1	1	-	-	-	-	-	-	-	-	-

 

25

IMPLEMENTATION AS MINIMIZED SUM-OF-PRODUCTS (SOP)

- 15 unique product terms when minimized individually

		A		
	1	0	X	1
	0	1	X	1
C	1	1	X	X
	1	1	X	X
		B		

		A		
	1	1	X	1
	1	0	X	1
C	1	1	X	X
	1	0	X	X
		B		

		A		
	1	1	X	1
	1	1	X	1
C	1	1	X	X
	0	1	X	X
		B		

		A		
	1	0	X	1
	0	1	X	0
C	1	0	X	X
	1	1	X	X
		B		

		A		
	1	0	X	1
	0	0	X	0
C	0	0	X	X
	0	1	X	X
		B		

		A		
	0	1	X	1
	0	1	X	1
C	1	0	X	X
	1	1	X	X
		B		

$$C0 = A + B D + C + B' D'$$

$$C1 = C' D' + C D + B'$$

$$C2 = B + C' + D$$

$$C3 = B' D' + C D' + B C' D + B' C$$

$$C4 = B' D' + C D'$$

$$C5 = A + C' D' + B D' + B C'$$

$$C6 = A + C D' + B C' + B' C$$

26

IMPLEMENTATION AS MINIMIZED SOP (CONT'D)

- Can do better
 - 9 unique product terms (instead of 15)
 - Share terms among outputs
 - Each output not necessarily in minimized form

		A			
C2		1	1	X	1
		1	1	X	1
	C	1	1	X	X
		0	1	X	X
		B			

$$\begin{aligned}
 C0 &= A + BD + C + B'D' \\
 C1 &= C'D' + CD + B' \\
 C2 &= B + C' + D \\
 C3 &= B'D' + C'D' + B'C'D + B'C \\
 C4 &= B'D' + C'D' \\
 C5 &= A + C'D' + BD' + BC' \\
 C6 &= A + CD' + BC' + B'C
 \end{aligned}$$

		A			
C2		1	1	X	1
		1	1	X	1
	C	1	1	X	X
		0	1	X	X
		B			

$$\begin{aligned}
 C0 &= BC'D + CD + B'D' + BCD' + A \\
 C1 &= B'D + C'D' + CD + B'D' \\
 C2 &= B'D + B'C'D + C'D' + CD + BCD' \\
 C3 &= B'C'D + B'D + B'D' + BCD' \\
 C4 &= B'D' + BCD' \\
 C5 &= B'C'D + C'D' + A + BCD' \\
 C6 &= B'C + BC' + BCD' + A
 \end{aligned}$$

27

IMPLEMENTATION AS MINIMIZED SOP (CONT'D)

- Can do better
 - 9 unique product terms (instead of 15)
 - Share terms among outputs
 - Each output not necessarily in minimized form

		A			
C2		1	1	X	1
		1	1	X	1
	C	1	1	X	X
		0	1	X	X
		B			


$$\begin{aligned}
 C0 &= A + BD + C + B'D' \\
 C1 &= C'D' + CD + B' \\
 C2 &= B + C' + D \\
 C3 &= B'D' + C'D' + B'C'D + B'C \\
 C4 &= B'D' + C'D' \\
 C5 &= A + C'D' + BD' + BC' \\
 C6 &= A + CD' + BC' + B'C
 \end{aligned}$$

		A			
C2		1	1	X	1
		1	1	X	1
	C	1	1	X	X
		0	1	X	X
		B			

$$\begin{aligned}
 C0 &= BC'D + CD + B'D' + BCD' + A \\
 C1 &= B'D + C'D' + CD + B'D' \\
 C2 &= B'D + B'C'D + C'D' + CD + BCD' \\
 C3 &= B'C'D + B'D + B'D' + BCD' \\
 C4 &= B'D' + BCD' \\
 C5 &= B'C'D + C'D' + A + BCD' \\
 C6 &= B'C + BC' + BCD' + A
 \end{aligned}$$


28

PLA IMPLEMENTATION

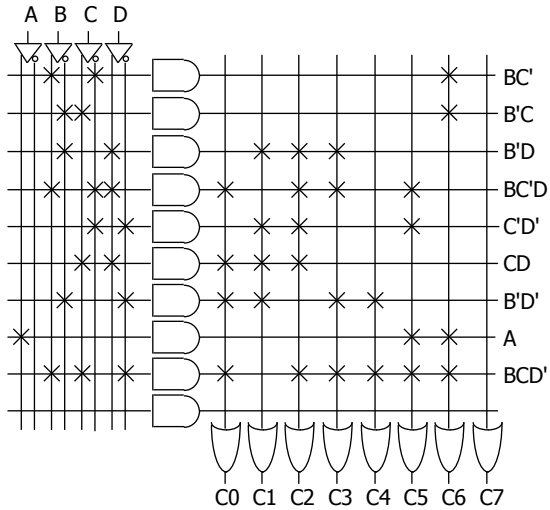

29

 AND-OR-XOR LOGIC DEMO EXAMPLE: BCD-TO-GLIXON CODE CONVERSION



Design a (normal) BCD/Glixon code converter. The illegal code words cannot be present at the inputs.

30

EXAMPLE (EXCLUSIVE-OR LOGIC): BCD-TO-GLIXON CODE CONVERTER

The Glixon code is a one-step BCD code (the Hamming distance is 1). The code words from 0 to 9 are

0000(0)	0001(1)	0011(2)	0010(3)	0110(4)
0111(5)	0101(6)	0100(7)	1100(8)	1000(9)

Normal BCD code: ABCD (A is the MSB)

Glixon code: E3, E2, E1, E0 (E3 is the MSB).

$$E3 = \sum(8,9)X(10-15)$$


$$E2 = \sum(4-8)X(10-15)$$

$$E1 = \sum(2-5)X(10-15)$$

$$E0 = \sum(1,2,5,6)X(10-15)$$

31

MINIMIZED TWO LEVEL AND-OR CIRCUIT

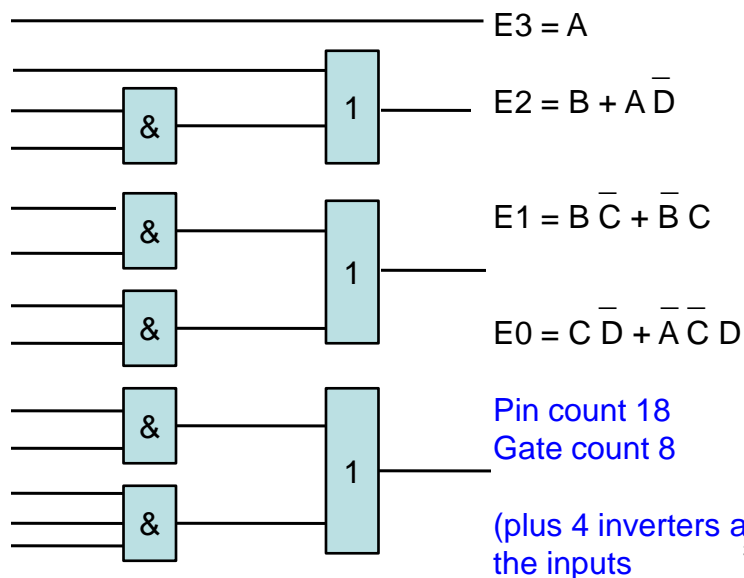

32

AND-OR-EXCLUSIVE-OR LOGIC IMPLEMENTATION


Using XOR gates in implementing (partially) symmetric logic functions make possible to obtain more economical solutions than using standard optimized two-level AND-OR or OR-AND circuits.

Here this approach can be applied to E1 and E0.

Full or partial symmetry is evident on the Karnaugh map by noting the chessboard patterns.


33

AND-OR-XOR LOGIC: E1

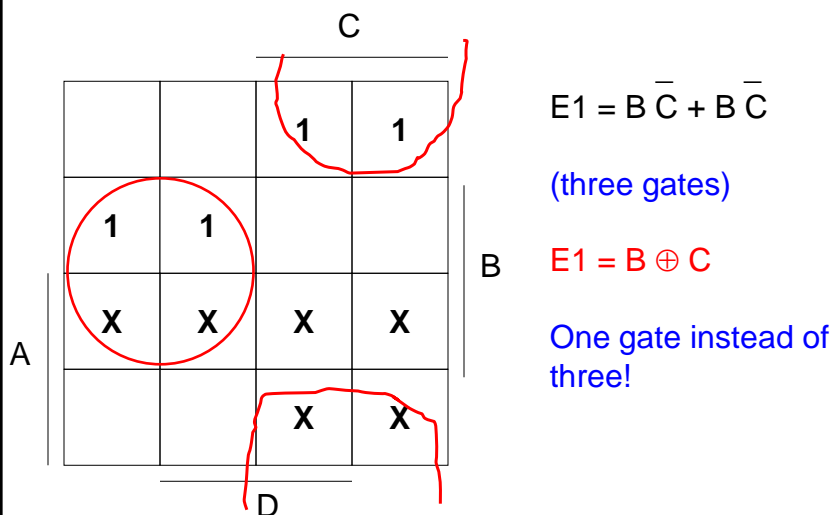


34

AND-OR-XOR LOGIC: E0

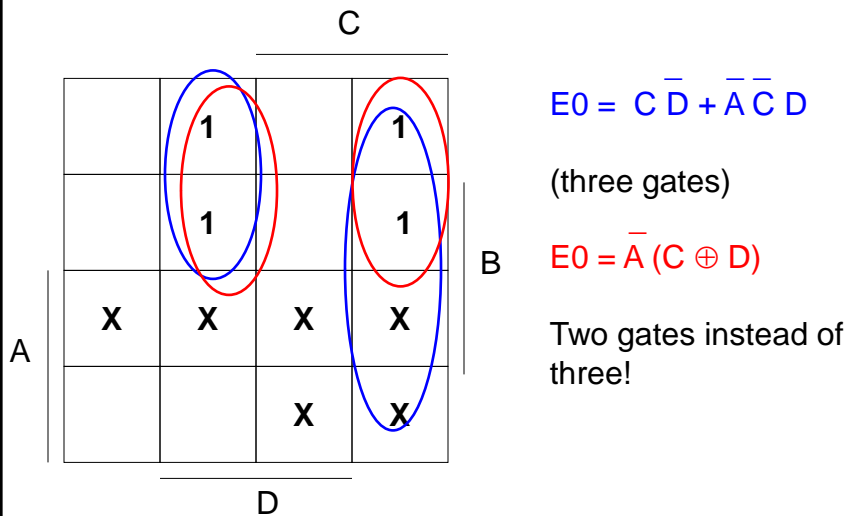

35

AND-OR-XOR LOGIC IMPLEMENTATION

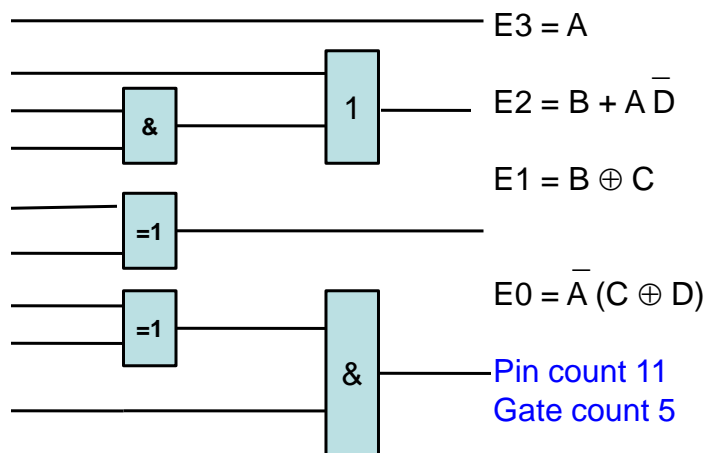

Additional benefit: 2 inverters instead of 4 at the input!

36

2-LEVEL AND/OR VERSUS AND/OR/XOR

Comparison of the two approaches (including input inverters where necessary):

	two-level AND/OR	(three-level) AND/ORXOR
Pin count	18	11
Gate count	8	5
Input inverters	4	2

COMBINATIONAL LOGIC DESIGN USING FUNCTIONAL BLOCKS

The traditional process of logic synthesis is based on the application of logic gates.

However in many case it is more advantageous to use a logic synthesis procedure based on the application of logic functional blocks.

Demo examples:

- Functional units (multiplexer, decoder) as building blocks
- Logical function unit
- Mux based shifter

DIGITAL SYNTHESIS: BUILDING BLOCKS

Lower level of abstraction: gates


Higher hierarchy: functional building blocks

Encoders, decoders
 Multiplexers, demultiplexers
 Registers, memories
 Comparators
 Adders, etc. (binary arithmetic blocks)

Programmable logic devices

Technological realization: SSI/MSI circuits

FAMILY TREE OF FUNCTIONAL BLOCKS

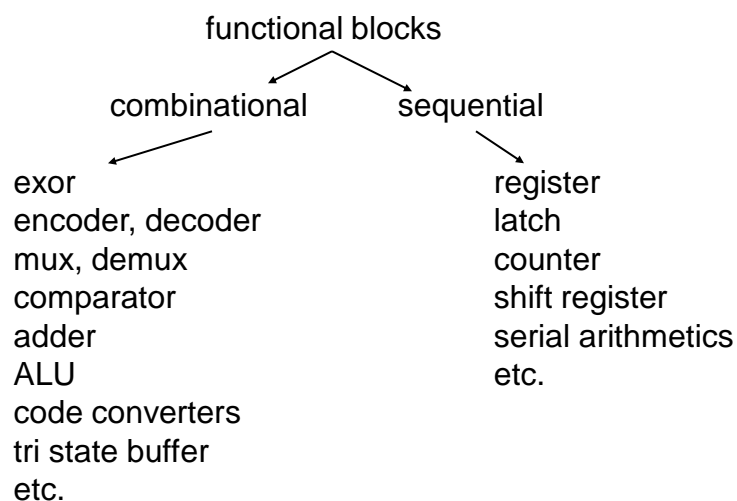

DIGITAL COMPONENTS

High level digital circuit designs are normally made using collections of logic gates referred to as components, rather than using individual logic gates.

Levels of integration (numbers of gates) in an integrated circuit (IC):

Small scale integration (**SSI**): about 10 gates.

Medium scale integration (**MSI**): 10 to 100 gates.

Large scale integration (**LSI**): 100-1,000 logic gates.

Very large scale integration (**VLSI**): 1,000-upward.

Ultra large scale integration (**ULSI**): 10,000-upward.

Giga large scale Integration (**GLSI**): 100, 000 upward.

Ridiculously (?) large scale integration (**RLSI**): 1,000,000 upward.

These levels are approximate, but the distinctions are useful in comparing the relative complexity of circuits.

What we need to know about an MSI circuit?

- *Function*: what it does
- *Truth-table*: input-output
- *Logic gate diagram*: how it does it
- *Packaging* (module pin-out): how to build it
- *Dynamic behavior* (timing diagram)
- *Applications*: where to use it


Common MSI circuits:

programmable logic devices (PLDs)
 encoder, decoder, exor, comparator,
 mux, demux, adder, subtractor,
 arithmetic circuits (adders, multipliers)
 Arithmetic and Logic Unit (ALU)

DECODER APPLICATION: IMPLEMENTING BOOLEAN FUNCTIONS USING DECODERS

- Any combinational circuit can be constructed using decoders and OR gates!
- Example: Implement a full adder circuit with a decoder and two OR gates.
- Recall full adder equations, and let X, Y, and Z be the inputs:
 - $S(X,Y,Z) = X+Y+Z = \Sigma m(1,2,4,7)$
 - $C(X,Y,Z) = \Sigma m(3, 5, 6, 7)$.
- Since there are 3 inputs and a total of 8 minterms, we need a 3-to-8 decoder.

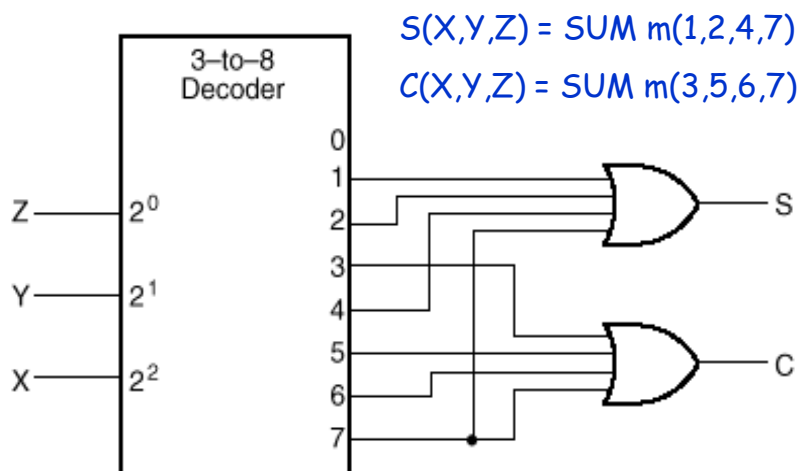IMPLEMENTING A BINARY ADDER USING A DECODER



MULTIPLEXER AS AN UNIVERSAL COMBINATIONAL CIRCUIT

From the point of view of output(s) the multiplexer can be considered as a one level combinational circuit.


Its characteristics is the fast response time.

For the selected input the time delay corresponds to the unit gate delay.


MULTIPLEXER BASED IMPLEMENTATION OF XOR FUNCTION

$$F = A\bar{B} + \bar{A}B$$

<i>A</i>	<i>B</i>	<i>F</i>
0	0	0
0	1	1
1	0	1
1	1	0

 


 USING A 4-1 MUX TO IMPLEMENT THE MAJORITY FUNCTION



Principle: Use the A and B inputs to select a pair of minterms. The value applied to the MUX input is selected from $\{0, 1, C, C'\}$ to pick the desired behaviour of the minterm pair.

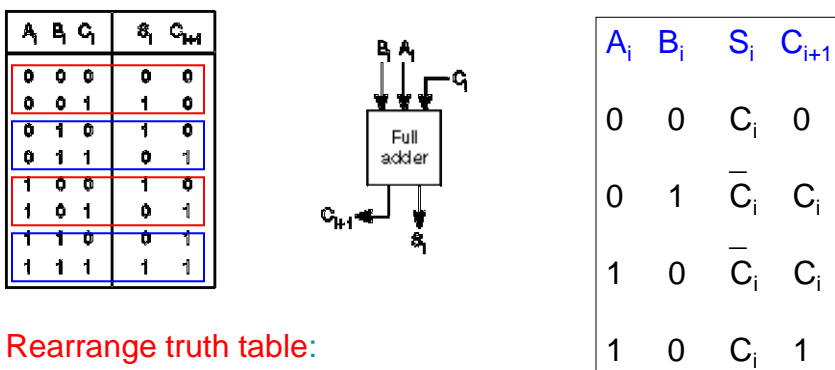EXAMPLE: USING MULTIPLEXER TO IMPLEMENT AN ADDER




Rearrange truth table:

Use A_i, B_i to select MUX output, connect C_i and C_i' to MUX data inputs.

Implement with two 4-to-1 multiplexers and one inverter (to generate C_i')

1-BIT FULL ADDER: MUX IMPLEMENTATION

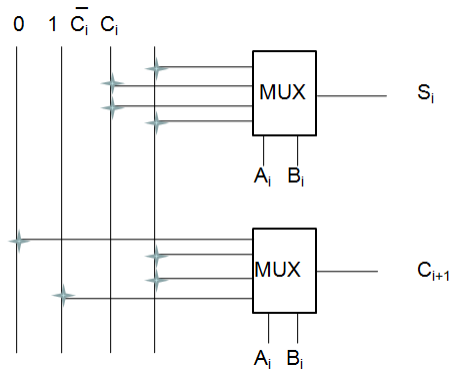

74153 dual 4-line to 1-line data selector/multiplexer.

Two 4/2/1 multiplexers in one package.

An inverter is also necessary (e.g. 1/6 7404 hex inverter).

49

EXAMPLE: MULTI PURPOSE FUNCTION BLOCK

• Multi-purpose Function Block

- 3 control inputs to specify operation to perform on operands
- 2 data inputs for operands
- 1 output of the same bit-width as operands

C_0	C_1	C_2	Function	Comments
0	0	0	1	always 1
0	0	1	$A + B$	logical OR
0	1	0	$(A \bullet B)'$	logical NAND
0	1	1	$A \text{ XOR } B$	logical XOR
1	0	0	$A \text{ XNOR } B$	logical XNOR
1	0	1	$A \bullet B$	logical AND
1	1	0	$(A + B)'$	logical NOR
1	1	1	0	always 0

3 control inputs: C_0 , C_1 , C_2

2 data inputs: A , B

1 output: F

IMPLEMENTATION WITH LOGIC GATES

C0	C1	C2	A	B	F
0	0	0	0	0	1
0	0	0	0	1	1
0	0	0	1	0	1
0	0	0	1	1	1
0	0	1	0	0	0
0	0	1	0	1	1
0	0	1	1	0	1
0	0	1	1	1	1
0	1	0	0	0	1
0	1	0	0	1	1
0	1	0	1	0	1
0	1	0	1	1	0
0	1	1	0	0	0
0	1	1	0	1	1
0	1	1	1	0	1
0	1	1	1	1	0
1	0	0	0	0	1
1	0	0	0	1	0
1	0	0	1	0	0
1	0	0	1	1	1
1	0	1	0	0	0
1	0	1	0	1	0
1	0	1	1	0	0
1	0	1	1	1	1
1	1	0	0	0	1
1	1	0	0	1	0
1	1	0	1	0	0
1	1	0	1	1	0
1	1	1	0	0	0
1	1	1	0	1	0
1	1	1	1	0	0
1	1	1	1	1	0

$$F = \Sigma^5(0-3,5-10,13,14,16,19,23,24)$$


Minimization on 5 variable
Karnaugh map:

four 4-cubes


FORMALIZE THE PROBLEM

C0	C1	C2	A	B	F
0	0	0	0	0	1
0	0	0	0	1	1
0	0	0	1	0	1
0	0	0	1	1	1
0	0	1	0	0	0
0	0	1	0	1	1
0	0	1	1	0	1
0	0	1	1	1	1
0	1	0	0	0	1
0	1	0	0	1	1
0	1	0	1	0	1
0	1	0	1	1	0
0	1	1	0	0	0
0	1	1	0	1	1
0	1	1	1	0	1
0	1	1	1	1	0
1	0	0	0	0	1
1	0	0	0	1	0
1	0	0	1	0	0
1	0	0	1	1	1
1	0	1	0	0	0
1	0	1	0	1	0
1	0	1	1	0	0
1	0	1	1	1	1
1	1	0	0	0	1
1	1	0	0	1	1
1	1	0	1	0	0
1	1	0	1	1	0
1	1	1	0	0	0
1	1	1	0	1	0
1	1	1	1	0	0
1	1	1	1	1	0

 choose implementation technology
5-variable K-map to discrete gates
multiplexer implementation
the target operations are pair wise
inverse of each other



MSI EXAMPLE: 74381/382 ALU

 


Eight-operation functional block ("limited" ALU) handling two 4-bit words.

Three logic operations, three arithmetic operations, clear and preset operations.

SN54LS381A, SN54S381, SN74LS381A, SN54LS382A, SN74LS382A, SN74S381 ARITHMETIC LOGIC UNITS/FUNCTION GENERATORS

- Fully Parallel 4-Bit ALUs in 20-Pin Package for 0.300-Inch Row Spacing
- Ideally Suited for High-Density Economical Processors
- 'LS381A and 'S381 Feature \bar{G} and \bar{P} Outputs for Look-Ahead Carry Cascading
- 'LS382A Features Ripple Carry ($C_n + 4$) and Overflow (OVR) Outputs
- Arithmetic and Logic Operations Selected Specifically to Simplify System Implementation:
 - A Minus B
 - B Minus A
 - A Plus B
 - and Five Other Functions

 


FUNCTION TABLE

SELECTION	ARITHMETIC/LOGIC		
S2	S1	S0	OPERATION
L	L	L	CLEAR
L	L	H	B MINUS A
L	H	L	A MINUS B
L	H	H	A PLUS B
H	L	L	$A \oplus B$
H	L	H	$A + B$
H	H	L	AB
H	H	H	PRESET

H = high level, L = low level

Gate-based logic

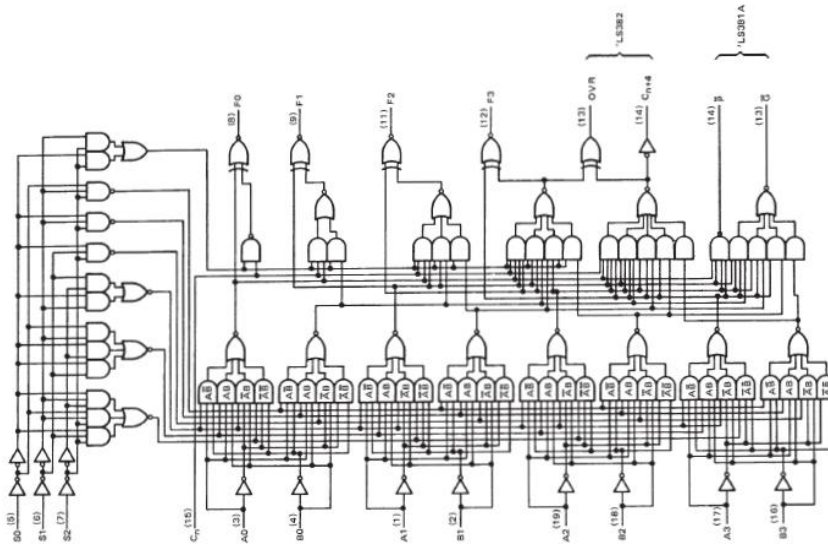SN54LS381A, SN54S381, SN74LS381A, SN54LS382A, SN74LS382A, SN74S381
ARITHMETIC LOGIC UNITS/FUNCTION GENERATORS



MUX BASED FUNCTIONAL (SUB-)UNITS

Data shifters and data rotators

Various logic functional units

Combinational adders/subtractors

Arithmetic logic unit (ALU)

Etc.

APPLICATION: MUX BASED SHIFTER

Draw a 4-bit shifter circuit for the following operation table using only six 2-to-1 multiplexers.

Operation table:


Shift left fill with 0 $A_3 A_2 A_1 A_0 \Rightarrow A_2 A_1 A_0 0$

Shift right fill with 0 $A_3 A_2 A_1 A_0 \Rightarrow 0 A_3 A_2 A_1$


Rotate left $A_3 A_2 A_1 A_0 \Rightarrow A_2 A_1 A_0 A_3$

Rotate right $A_3 A_2 A_1 A_0 \Rightarrow A_0 A_3 A_2 A_1$

57

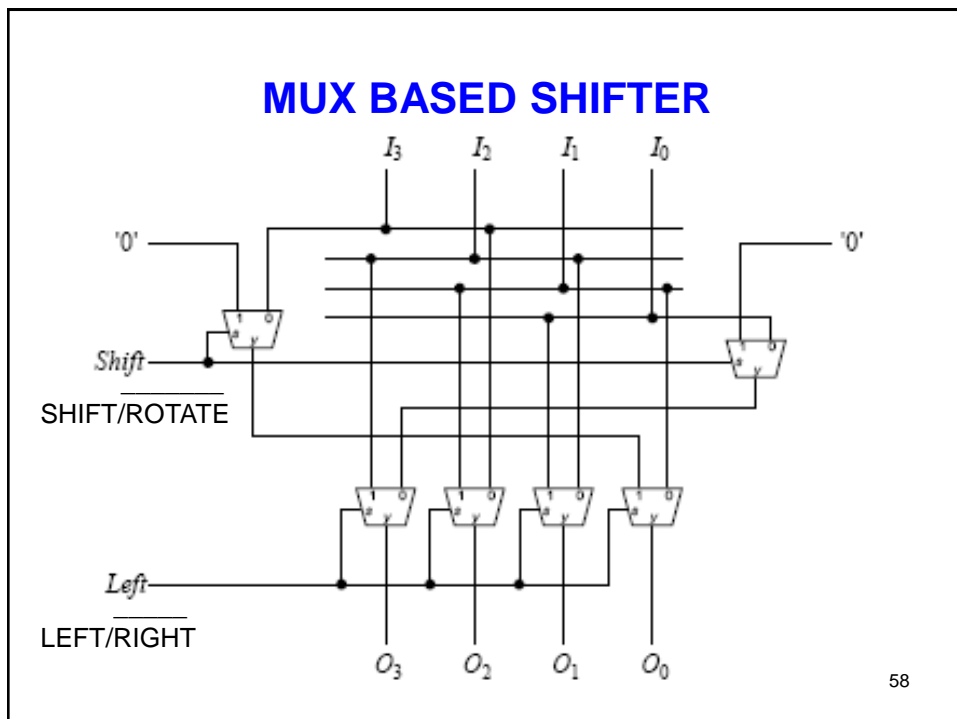


4-BIT LOGIC FUNCTION (AND, XOR) CIRCUIT

 


59

4-BIT ADDER/SUBTRACTOR CIRCUIT

 

60

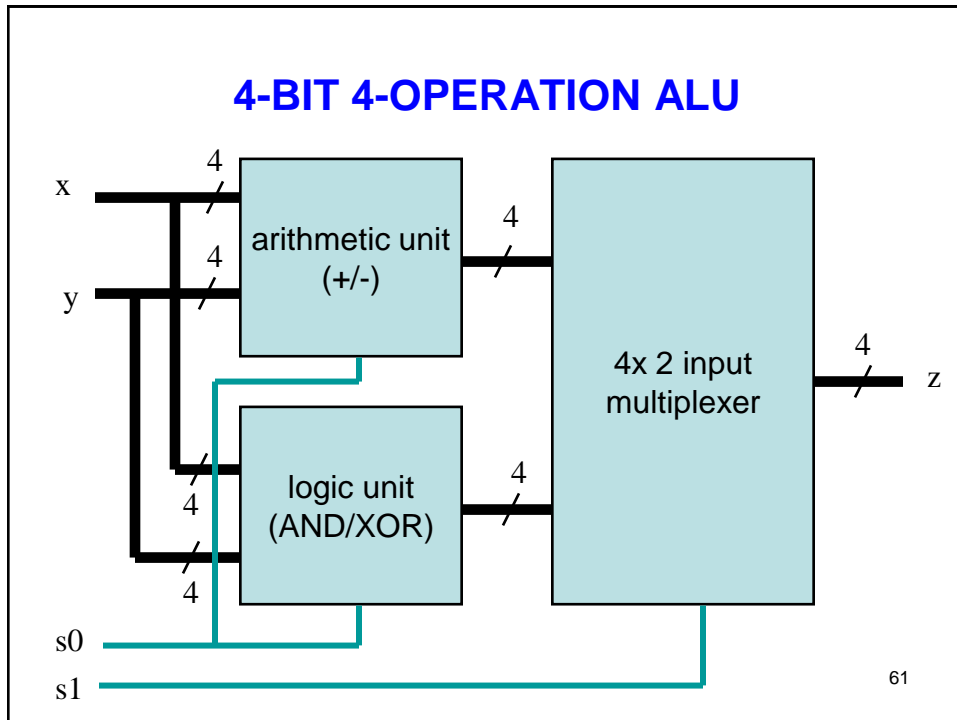

REVISION QUESTIONS

1. What is a multiplexer circuit? Briefly describe one or two applications of a multiplexer?
2. Is it possible to enhance the capability of an available multiplexer in terms of the number of input lines it can handle by using more than one device? If yes, briefly describe the procedure to do so, with the help of an example.
3. What is an encoder? How does a priority encoder differ from a conventional encoder? With the help of a truth table, briefly describe the functioning of a 10-line to four-line priority encoder with active LOW inputs and outputs and priority assigned to the higher-order inputs.

REVISION QUESTIONS


4. What is a demultiplexer and how does it differ from a decoder? Can a decoder be used as a demultiplexer? If yes, from where do we get the required input line?
5. Briefly describe how we can use a decoder optimally to implement a given Boolean function? Illustrate your answer with the help of an example.
6. What is a look-up table (LUT)? How can it be used to implement a combinational logic function?
7. Present the layout of the two's complement adder/subtractor and explain its operation.

PROBLEMS AND EXERCISES

1. Design, using only multiplexers (and inverters if necessary), a programmable logic gate, which depending on the logic value of the control line S , realizes either a two-input EXCLUSIVE-OR function, or a two-input NAND function.
2. Implement the 1-bit full subtractor using 4-to-1 multiplexers.
3. A 4-to-1 multiplexer has signals A and B connected to the selection inputs S_1 and S_0 , respectively. The data inputs I_0 through I_3 , are as follows: $I_1 = 0$, $I_2 = 1$, $I_0 = C$; and $I_3 = C'$ (C -bar). Determine the Boolean function $F(A,B,C)$ that the multiplexer implements.

PROBLEMS AND EXERCISES

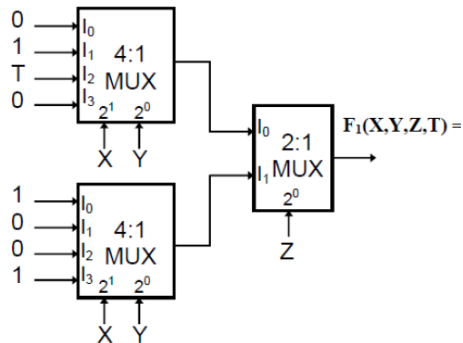4. Draw the logic diagram of a 2-to-4 line decoder using NOR gates only. Include an enable input.
5. Determine the Boolean function of the output of the multiplexer circuit shown below.



END OF LECTURE