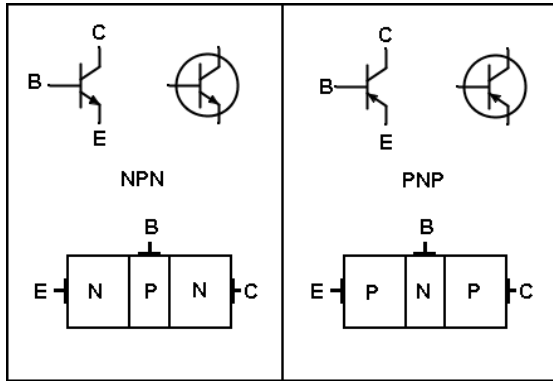



# 1. Bipolar junction transistor

## 1.1. Intro

### 1.1.1. Symbols, structure



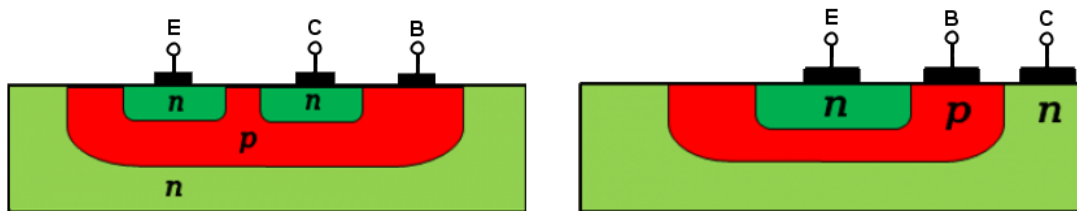
1.: Symbols and simplified structure (order of layers) (left: NPN, right: PNP)



2.: Left: Planar structure NPN. Right: Lateral structure NPN transistor.

The figures show that the emitter and collector layers are of different size and geometry. They also have different doping concentrations. Therefore, the E and C are not wholly interchangeable in circuits (the transistor parameters will suffer if doing so).


### 1.1.2. Characteristics

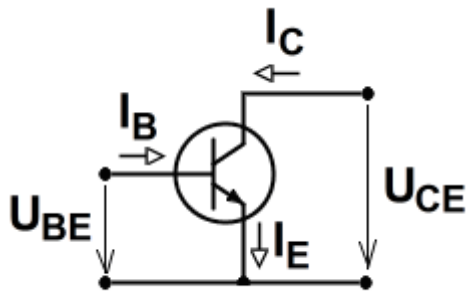

#### 3.: Common Emitter (CE) model

Remember: in practice, do not connect a voltage source directly parallel to BE junction (or to CB junction), without resistor or current limit.

*Input characteristic of CE model:*

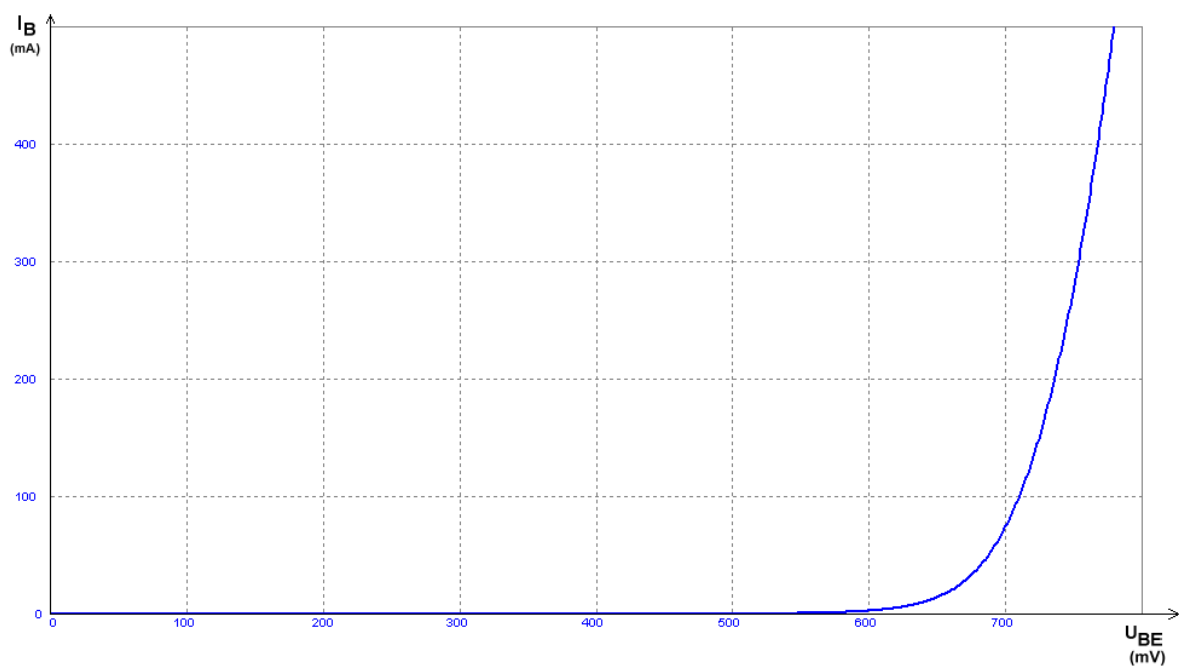

#### 4.: $V_{BE}$ - $I_B$ characteristics, forward region, fix temperature

Remember also that the figures here are just examples. The actual transistors' parameters may slightly vary.


As the BE junction is forward biased, the diode equation can be used here:

$$I_B = I_{B0} \cdot \left( e^{\frac{V_{BE}}{V_T}} - 1 \right)$$

where  $I_{B0}$  is the reverse current (or drift current) (very very small, typically pA magnitude) and  $V_T$  is the thermal voltage (26mV at room temperature), both temperature dependent.

As with diodes, the characteristic curve is temperature dependent. At higher temperature, the function values ( $I_B$ ) are multiplied. Looking at the curve, it looks like as if the curve is moving to the left (except that it still crosses the origin). At a fix current, it looks as if the curve moves about -2mV per Kelvin, ie. it moves to the left with increasing temperature. Therefore there is a risk of thermal runaway and thus the warning to not connect a voltage source (without current limit) parallel to the forward biased PN junction.

### *CE output characteristic*

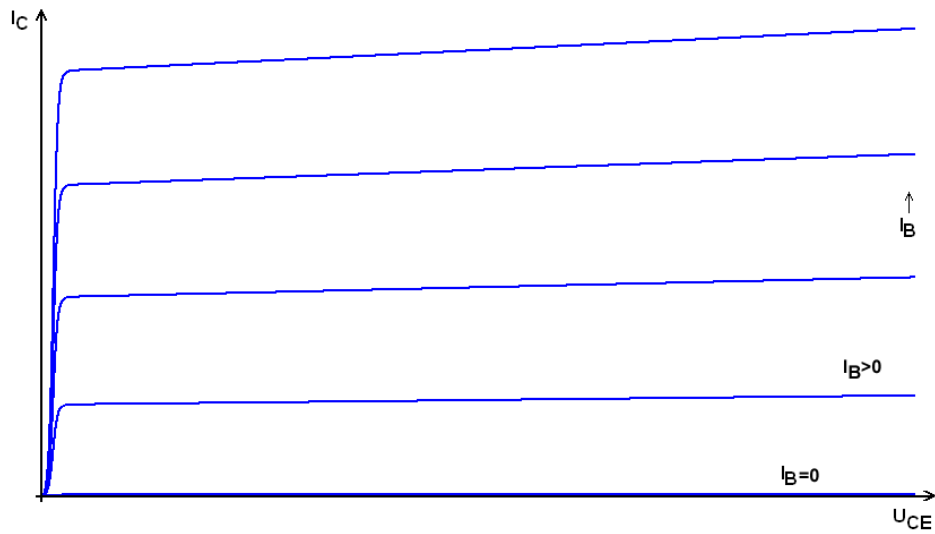


#### 5.: $V_{CE}$ - $I_C$ curve

Here we get different  $V_{CE}$ - $I_C$  curves for different base currents.  $I_C$  is close to zero (see the drift current of the diode) when  $I_B$  is zero.

If  $V_{CE}$  is sufficiently large (usually after a few hundred mV or a few V), the curve becomes relatively flat, here it behaves as a current generator. In this section we can use the transistor as current generator or as amplifier.
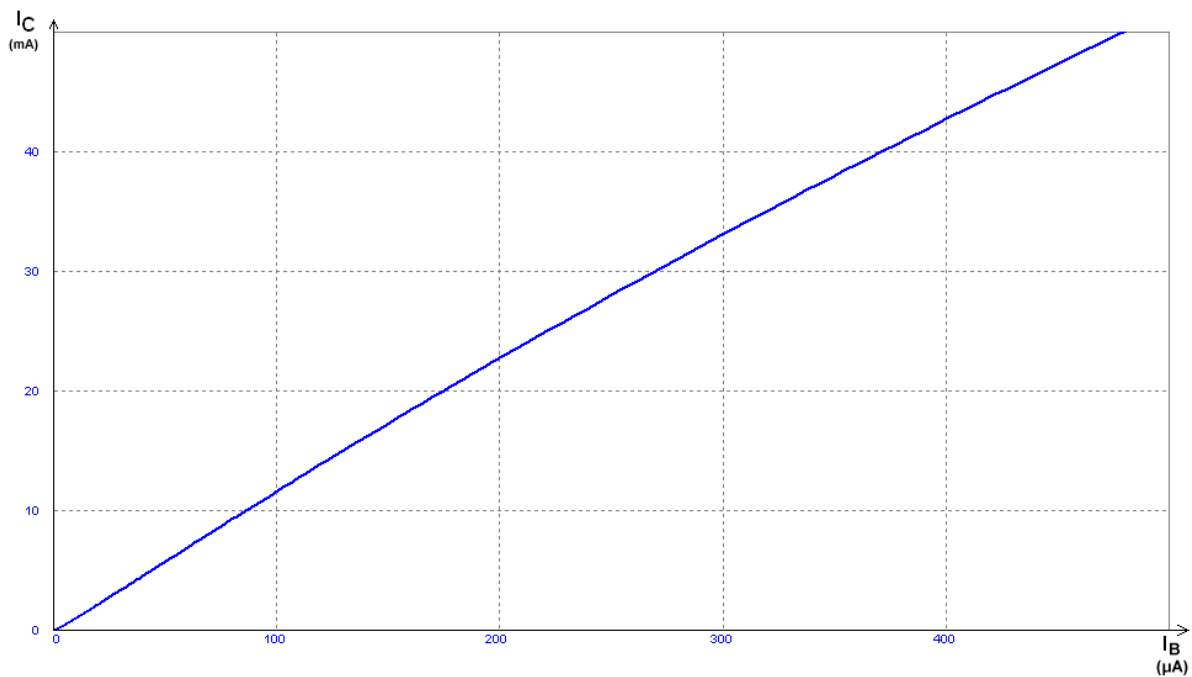
### ***I<sub>C</sub>-I<sub>B</sub> characteristic (current transfer char.)***



#### **6.: $I_C$ - $I_B$ curve**

If we have forward bias on  $V_{BE}$  and  $V_{CE}$  is large enough (to be in the current generator section), then  $I_C$  and  $I_B$  are approximately linearly proportional:

$$I_C = B \cdot I_B$$

Don't forget that we need a power supply to get this! The transistor can not make higher output current out of air.

The  $B$  (capital beta) current gain is ideally constant. For modern low current (typ.  $<1\text{A}$ ) transistors the value of  $B$  is between about 100 to 600 (meaning it has a very large tolerance, ie. manufacturing uncertainty). For high current transistors at large  $I_C$  and also for very old transistors the  $B$  can be much lower, a few ten or less. The curve thus "flattens out" at higher currents.

Node law says:

$$I_C + I_B = I_E$$

therefore

$$B \cdot I_B + I_B = I_E$$

$$(B+1) \cdot I_B = I_E$$

Reorganise and introduce constant A (alpha), which is ratio of  $I_C$  and  $I_E$ :

$$(B+1) \cdot \frac{I_C}{B} = I_E$$

$$\frac{B+1}{B} I_C = I_E$$

$$I_C = \frac{B}{B+1} I_E$$

$$I_C = A \cdot I_E$$

$$A = \frac{B}{B+1}$$

If  $B > 100$ , then  $A > 0.99$ , thus we can safely say that  $I_E = I_C$ . (Note: at  $B=100$ ,  $A=0.99$ . At  $B=200$ ,  $A=0.995$ . At  $B=400$ ,  $A=0.9975$ . Thus large variations in beta result in negligible change in alpha. Therefore in this regard, we can safely ignore the tolerance of B as long as it's large enough. It requires a carefully designed circuit though, where the output depends on A instead of B.)


### ***$V_{BE}$ - $I_C$ transfer characteristic***

With proper voltage applied on both VBE and VCE, we can work the previous characteristics together to get the transfer curve. As  $I_C = \beta I_B$ , it will look similar to the input curve:

$$I_C = I_{C0} \cdot e^{\frac{U_{BE}}{U_T}}$$

(Note the -1 is missing, as  $I_C$  will have the  $I_{C0}$  drift current even when  $I_B$  is zero.)

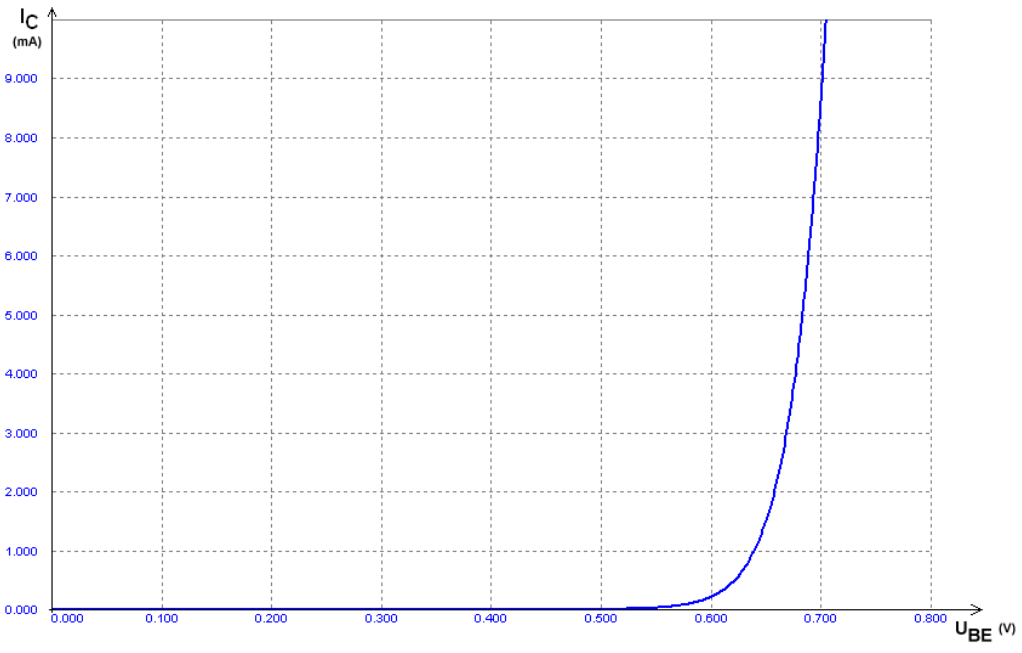Remember that this equation is only true as long as VCE is large enough (in the saturated (current generator) section).




7.  $V_{BE}$ - $I_C$  transfer curve

## 1.2. Setting the operating point

For several reasons it is advisable to include a resistor connected to the BE junction. It can either be connected from base or from emitter.

### 1.2.1. Base resistor method

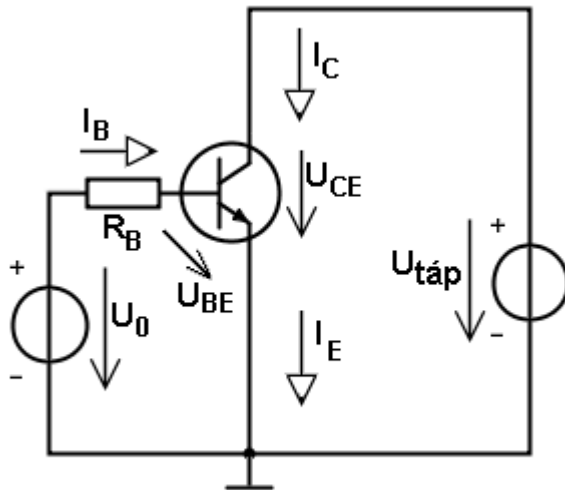

#### 8. Base resistor / base current setting

If  $V_0$  is larger than the forward voltage, we can assume  $V_{BE}=0.7V$ .  
Then

$$V_{R_B} = V_0 - V_{BE} = V_0 - 0.7V$$

$$I_B = \frac{V_{R_B}}{R_B} = \frac{V_0 - 0.7V}{R_B}$$


$$I_C = B \cdot I_B$$

$$I_E = A \cdot I_C \approx I_C$$


Here the  $I_C$  will depend on  $B$ . That is usually not acceptable, as  $B$  has a very large uncertainty. This method is thus not used in current generators or amplifiers generally. It can be used in switching mode.


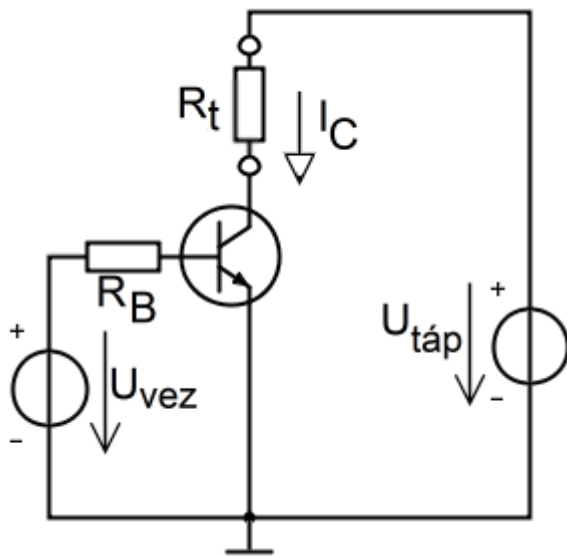
### Base resistor method in switching mode




9. Switching mode ( $R_t$  is the load)

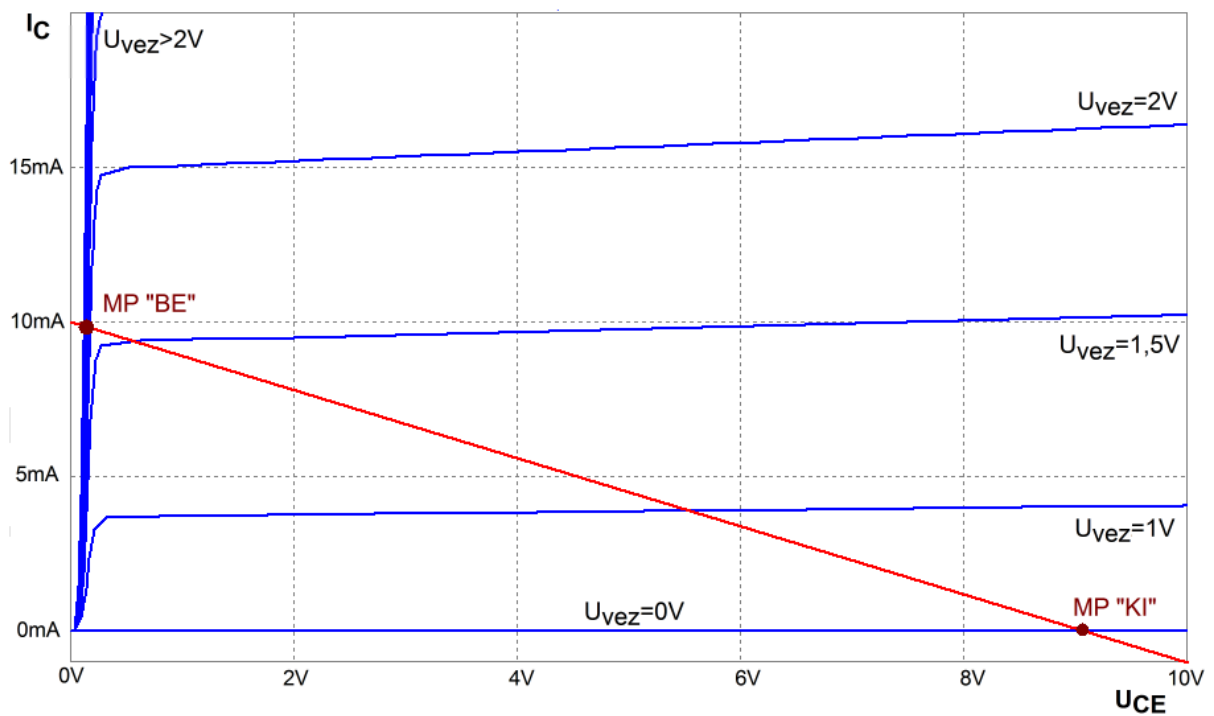

10. Switching mode. Red curve is the resistor's characteristic. (KI=On, BE=Off, MP=Operating Point)

### 1.2.2. Emitter resistor method

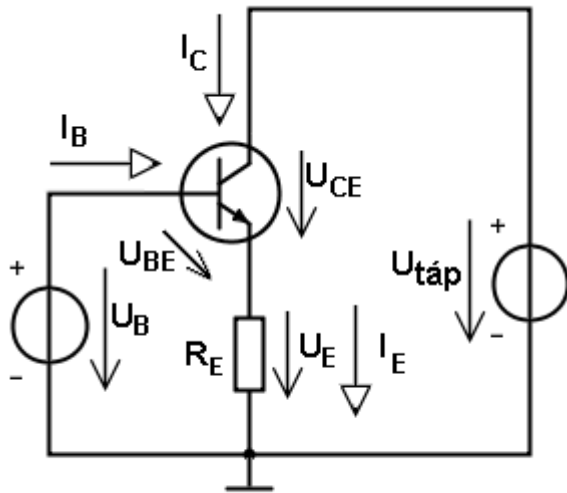

#### 11. Operating point setup with emitter resistor (1)

$$V_{BE} = 0.7V$$

$$V_E = V_B - V_{BE}$$

$$V_{CE} = V_{táp} - V_E$$

$$I_E = \frac{V_E}{R_E}$$

$$\text{if } B \gg 1 \text{ (} B > 100 \text{)} \Rightarrow I_B \ll I_C \Rightarrow I_C \approx I_E$$

$$I_B = \frac{I_C}{B}$$

Here  $I_C$  doesn't depend on  $B$ , only on the uncertainty of  $V_{BE}$  (much better) (and on  $A$ , but that is really negligible usually). Here the  $I_B$  will depend on  $B$ , but that is usually not a problem (the output quantity is usually  $I_C$  or related to it).

The larger  $V_E$  and  $R_E$ , the more precisely  $I_C$  can be set, the lower the effect of the uncertainty of the forward voltage.

#### Example

Let's use these values for an example calculation:

$V_B = 4.7V$  ;  $R_E = 2k\Omega$ ,  $V_{supply} = 10V$  (only important thing now is  $V_{supply} > V_B$ ).

For example a BC182 transistor datasheet says  $V_{BE}$  is between 0.55V and 0.7V when  $I_C = 2mA$ .

First suppose that the given maximum,  $V_{BE1} = 0.7V$  will be true value.

$$V_B = 4,7V$$

$$V_{BE1} = 0,7V$$

$$V_{E1} = V_B - V_{BE1} = 4V$$

$$I_{E1} = \frac{V_{E1}}{R_E} = \frac{4V}{2k\Omega} = 2mA$$

Now what if  $V_{BE}$  is different actually? Let's use now the minimum given value:

$$V_{BE2} = 0,55V.$$

$$V_B = 4,7V$$

$$V_{BE2} = 0,55V$$

$$V_{E2} = V_B - V_{BE2} = 4,15V$$

$$I_{E2} = \frac{V_{E2}}{R_E} = \frac{4,15V}{2k\Omega} = 2,075mA$$

The relative difference between the two calculated emitter currents:

$$I_{E1} = 2mA$$

$$I_{E2} = 2,075mA$$

$$\frac{\Delta I_E}{I_{E2}} = \frac{I_{E2} - I_{E1}}{I_{E2}} = \frac{0,075mA}{2mA} = 0,0375 = 3,75\%$$

Thus 150mV difference in the estimation of  $V_{BE}$  (21..27%) will result in 3.75% change in the emitter current. If we used twice the  $V_B$  and twice the  $R_E$ , then  $I_E$  would be the same, but the uncertainty of it only half.

This is why the estimation of  $V_{BE}$  to be 0.6V ... 0.7V is usually acceptable.

### **The emitter resistor also acts a negative feedback.**


Suppose for example, that the transistor's temperature increases. If our  $V_{BE}$  voltage is constant, then this would result in increased  $I_C$  and  $I_E$  (as the characteristic curve shifts left). The increased  $I_C$  would increase temperature even further, thus getting a positive feedback, a thermal runaway which would destroy the transistor.

If we have  $R_E$  in the circuit, then increased  $I_E$  results in increased  $V_E$ . But  $V_{BE} = V_B - V_E$ , so with constant  $V_B$ ,  $V_{BE}$  will decrease. But if  $V_{BE}$  decreases, then - according to the transfer characteristic curve -  $I_C$  and  $I_E$  will decrease. We started from  $I_C$  and  $I_E$  increasing, which then lead to an effect of them decreasing. The two effects try to cancel each other out. (Obviously decreasing  $I_C$  would lead to increase.)

Therefore we have a negative feedback. This tries to keep  $I_C$  and  $I_E$  at near constant value.

This effect works regardless of the reason for change of  $I_C$ . It could be the change of  $R_C$  ( $R_L$ ) in a current generator. It could be from AC input signal on the base of the amplifier as well, which means that if we have a common emitter amplifier with  $R_E$  but without  $C_E$ , then the negative feedback will make the output AC signal very small, ie. it will decrease the voltage gain (compared to the original circuit with  $C_E$ ).

## Current generator

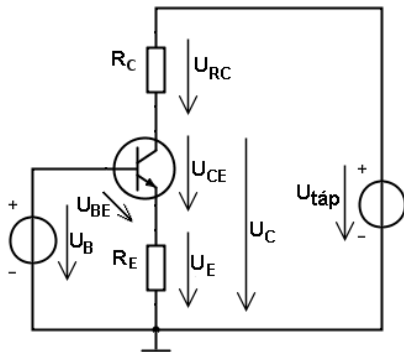

### 12.: Model of current generator


Now we see that the transistor can be used as a current generator if used in the "flat" section of the output characteristic. The emitter resistor has two roles here: first, it allows setting up  $I_C$  independently of value of (uncertainty of)  $\beta$  and greatly decreases the effect of uncertainty of  $V_{BE}$ . Second, it provides the negative feedback which tries to keep  $I_C$  from changing, which adds to the already existing effect of being a current generator - in effect, it tries to make the output curve even flatter.

The collector potential is calculated as:

$$V_C = V_{\text{supply}} - I_C R_C$$

Remember, the  $\perp$  symbol here denotes the reference zero for node potentials. Symbols with one letter index, such as  $V_C$ , indicate node potentials. Symbols with two indices indicate voltages between those points, like  $V_{CE}$ . So  $VC$  could be written also as  $V_{C0}$ .

### Using double power supply

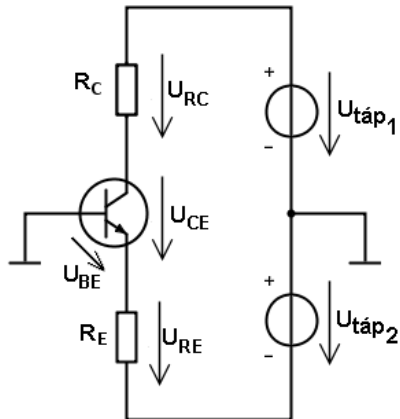

#### 13. Using double power supply

In this case we use two voltage generators to provide a + and a - voltage relative to the zero (which is now between the two generators and indicated by the  $\perp$  symbol).

In this case,  $V_E$  and  $V_{RE}$  are different, as the bottom of  $R_E$  is at negative potential, not zero.

If for example  $V_{\text{supply1}}=10\text{V}$ ,  $V_{\text{supply2}}=5\text{V}$ ,  $R_E=R_C=1\text{k}\Omega$ :

$$V_E = 0 - V_{BE} = -0,7\text{V}$$

$$V_{RE} = V_E - (-V_{\text{supply2}}) = -0,7 - (-5) = 4,3\text{V}$$

$$I_E = \frac{V_{RE}}{R_E} = \frac{4,3\text{V}}{1\text{k}\Omega} = 4,3\text{mA}$$


$$I_C \approx I_E$$

$$V_{RC} = I_C R_C = 4,3\text{V}$$

$$V_C = V_{\text{táp1}} - V_{RC} = 10\text{V} - 4,3\text{V} = 5,7\text{V}$$

For  $R_C$  and  $V_C$ , it behaves similarly to the previous circuit.

### 1.3. Current generator

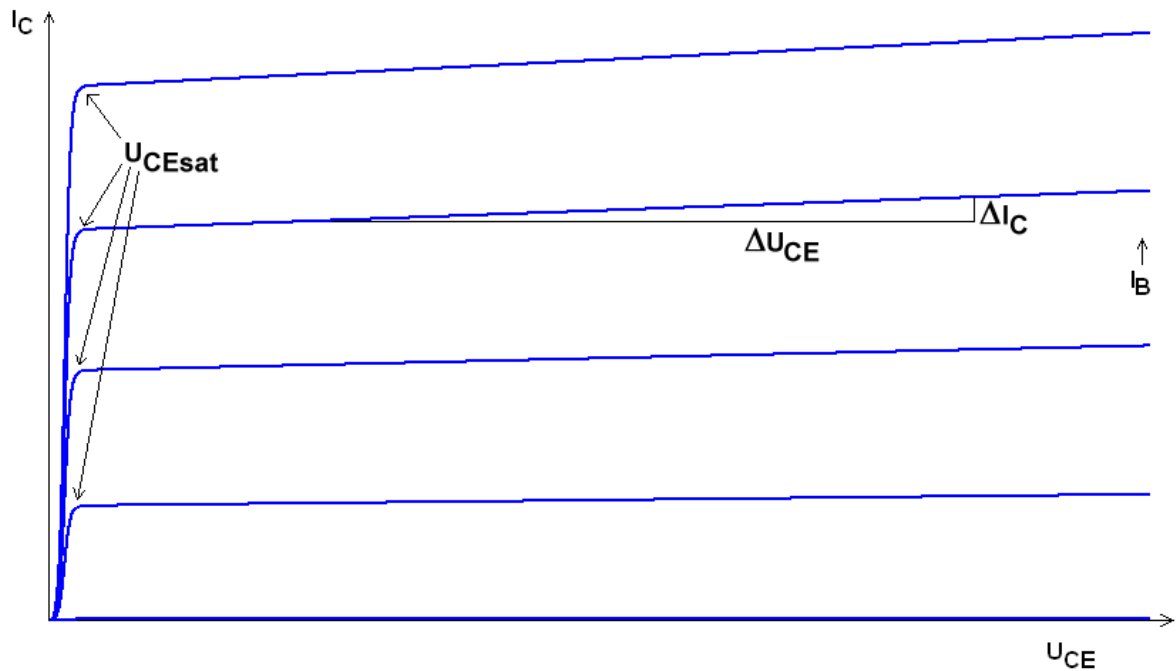

#### 14. $V_{CEsat}$ and $r_{CE}$ explanation


The quality of the current generator (how constant is  $I_C$ ) depends on the "flatness" (slope) of the VCE- $I_C$  curve, ie. the dynamic output resistance of the transistor.

$$r_{CE} = \frac{dV_{CE}}{dI_C} \approx \frac{\Delta V_{CE}}{\Delta I_C}$$

In the right side of the curve this is seen to be very large (ie very flat). This can be from 30k $\Omega$  to 100k $\Omega$  or more. (Remember an ideal current generator has infinite internal resistance.)  
As mentioned already, the RE as negative feedback makes the circuit's output resistance even greater than that provided by the transistor ( $r_{CE}$ ) itself.

$V_{CEsat}$  is the minimum voltage needed to reach the saturation (current generator mode). We can see this value is greater if  $I_C$  is greater. For low currents (few mA) this is usually a few hundred mV. For higher currents it could be volts.

## Current generator with double supply

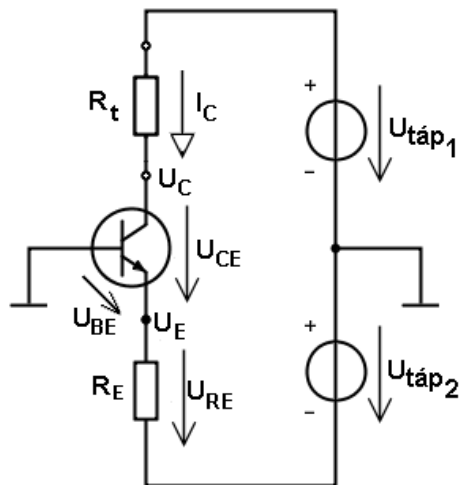

15.

$$U_E = 0 - U_{BE} = -0,7V$$


$$U_{RE} = U_E - (-U_{táp2})$$

$$I_E = \frac{U_{RE}}{R_E}$$

$$I_C \approx I_E \text{ (B nagy)}$$

Note: when writing  $V_{supply}$  ( $U_{táp}$  in Hungarian) next to a voltage arrow (next to a voltage generator), it is considered a voltage and is positive. But when used as a potential, it can be negative:  $V_{supply2}$  as potential (when written next to a node, in this case below the  $R_E$ ) will be negative, because its related generator is connected below the zero potential.

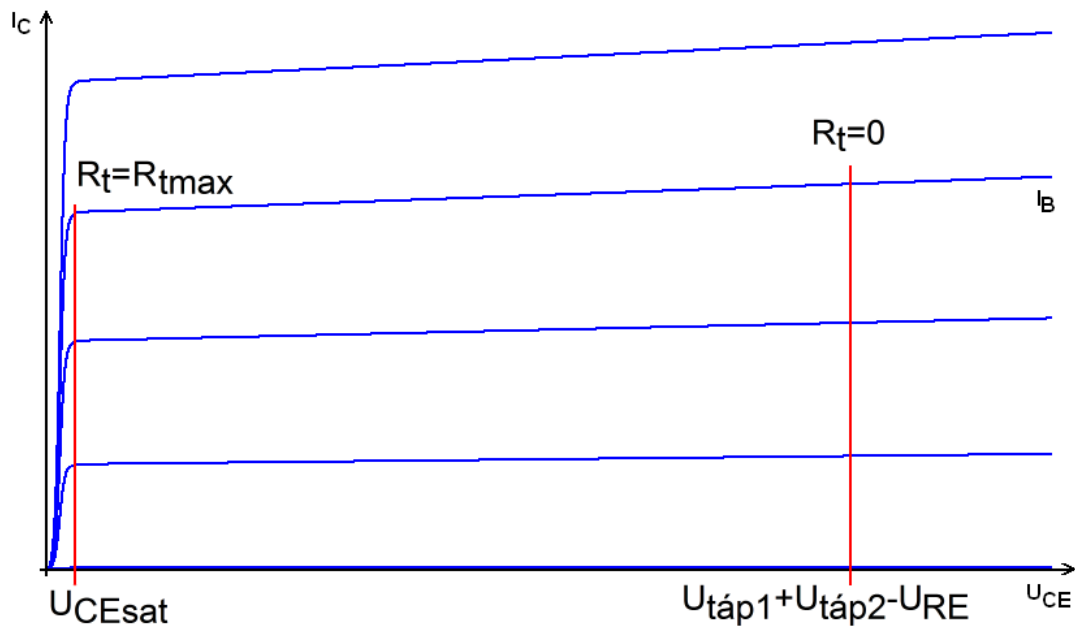Value of  $V_{supply2}$  is chosen similarly as  $V_B$  in the one supply version. It should be greater than  $V_{BE}$  (0.7V), possibly by several times, but not too much.



16.

What is the limit for the load resistor?

The ideal generator can be short circuited. Then the voltage on the load is zero. This works here, thus  $R_{Lmin}=0$ .

In this case

$$V_{CEmax} = V_{supply1} + V_{supply2} - V_{RE} = V_{supply1} + V_{supply2} - I_E \cdot R_E$$

(note:  $V_{supply1}$  and  $V_{supply2}$  are voltages here, all positive)

When increasing  $R_L$ , the current will only very slightly decrease due to the finite output resistance. But after reaching  $R_{Lmax}$ , the  $I_C$  will decrease strongly.

This happens when the voltage on the  $R_L$  becomes so great that there remains no sufficient voltage to bring the transistor  $V_{CE}$  into the saturated region (which requires minimum of  $V_{CEsat}$  voltage). When further increasing  $R_L$ , the potential  $V_C$  becomes lower than  $V_B$  and thus the C-B junction is forward biased, and current also flows from base to collector, subtracting from  $I_C$ .

If  $V_{CEsat}$  is known at the given  $I_C$  :

$$V_{RLmax} = V_{supply1} + V_{supply2} - V_{CEsat} - V_{RE} = V_{supply1} + V_{supply2} - V_{CEsat} - I_E \cdot R_E$$

$$R_{Lmax} = \frac{V_{RLmax}}{I_C} = \frac{V_{supply1} + V_{supply2} - V_{CEsat} - V_{RE}}{I_C}$$

Thus  $R_{Lmax}$  depends on power supply voltage and the saturation voltage.

In the double power supply circuit,  $V_E=-0,7V$  and thus:




$$V_{RLmax} = V_{supply1} + 0,7V - V_{CEsat}$$

$$R_{Lmax} = \frac{V_{RCmax}}{I_C} = \frac{V_{supply1} + 0,7V - V_{CEsat}}{I_C}$$

So  $R_{Lmax}$  only depends on  $V_{supply1}$ , not on  $V_{supply2}$ .
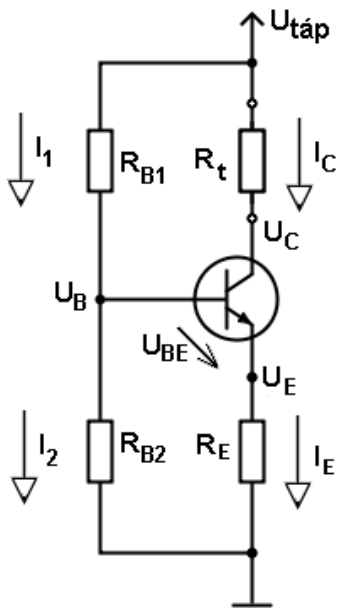
### 1.3.1. Current generator with one power supply



#### 17. Current generator

In practice, using two generators is expensive (cost, size, complexity). Therefore we replace  $V_{supply2}$  with a voltage divider. The simplest version is made from two resistors. Another version would use a resistor and a Zener-diode, this way it becomes almost independent from power supply value.

From now we use the up arrow to symbol the power supply potential, instead of showing the generator fully connected. This makes for easier overview of our circuits.

In this circuit,  $V_E = V_{RE}$  and  $V_B = V_{RB2}$ .

$$V_{RLmax} = V_{supply} - V_{CEsat} - V_E = V_{supply} - V_{CEsat} - I_E \cdot R_E$$

$$R_{Lmax} = \frac{V_{RLmax}}{I_C} = \frac{V_{supply} - V_{CEsat} - V_E}{I_C}$$

When designing, value of  $V_E$  can be chosen somewhat freely. Larger  $V_E$  means more precise setting of  $I_C$  but also lower  $R_{Lmax}$  and also higher power dissipation (counts if current is larger than a few hundred mA).

Values of  $R_{B1}$  and  $R_{B2}$  can be chosen also somewhat freely, as it's their ratio that counts. We have to make sure  $I_1 > I_B$  (as  $I_2 = I_1 - I_B$  and of course  $I_2$  should be positive).

$$I_1 = \text{choose } (I_1 > I_B)$$

$$I_2 = I_1 - I_B$$

$$R_1 = \frac{V_{\text{supply}} - V_B}{I_1}$$

$$R_2 = \frac{V_B}{I_2}$$

A usual practice for choosing  $I_1$  is

$$\text{let } I_1 = 10 \cdot I_B$$

$$\text{then } I_2 = I_1 - I_B = 9 \cdot I_B$$

When calculating an existing circuit, it is complicated to precisely calculate  $V_B$  and the result would still depend on B. Therefore we assume that the designer followed the above guideline and thus  $I_1 \gg I_B$  and we estimate  $V_B$  from voltage divider:

$$V_B \approx V_{\text{supply}} \frac{R_{B2}}{R_{B1} + R_{B2}}$$

*(Don't forget to check the validity of this estimation at the end.)*

From here:

$$V_E = V_B - 0,7V$$

$$I_E = \frac{V_E}{R_E}$$

$$I_C \approx I_E$$

Check:

$$I_B = \frac{I_C}{\beta}$$

$$I_1 = \frac{V_{\text{supply}} - V_B}{R_{B1}}$$

$$I_1 > 10 \cdot I_B \text{ ??}$$

### 1.3.2. Output resistance of current generator

As mentioned previously, the output resistance of the current generator depends on  $r_{CE}$  and on the feedback effect of  $R_E$ . To measure it:

$$r_{out} = \frac{dV_{out}}{dI_{out}} = \frac{dV_{RL}}{dI_C} \approx \frac{\Delta V_{RL}}{\Delta I_C}$$

This can tell us how much  $I_C$  changes if the load changes.

For example if  $R_L$  takes two possible extreme values  $R_{L1}$  and  $R_{L2}$ :


$I_C = 1\text{mA}$ ,  $r_{out} = 500\text{k}\Omega$ ,  $R_{L1} = 0$ ,  $R_{L2} = 1\text{k}\Omega$ .

Then (as long as  $R_{L2} < R_{Lmax}$ ) the change in  $I_C$ :

$$\Delta I_C = \frac{\Delta V_{RL}}{r_{out}} = \frac{R_L \Delta I_C + I_C \Delta R_L}{r_{out}} \approx \frac{I_C \Delta R_L}{r_{out}} = \frac{I_C (R_{L2} - R_{L1})}{r_{out}} = \frac{1\text{mA} \cdot 1\text{k}\Omega}{500\text{k}\Omega} = 2\mu\text{A}$$
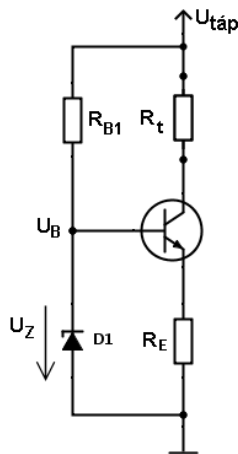
### 1.3.3. Current generator with Z-diode

In this case the Zener-diode tries to keep  $V_B$  somewhat constant even if  $V_{supply}$  changes (as long as  $V_{supply} > V_Z$  of course). This can be useful for example if the supply is fluctuating (like from a rectifier output) or is slowly decreasing (battery depleting).




#### 18. using Z-diode base divider

Make sure that the Z-diode gets minimum a few mA of current to properly work. (This is usually greater than what an R-divider would need).


## 1.4. Simple amplifier circuits

### 1.4.1. Common Emitter (CE) amplifier

*The amplification process*

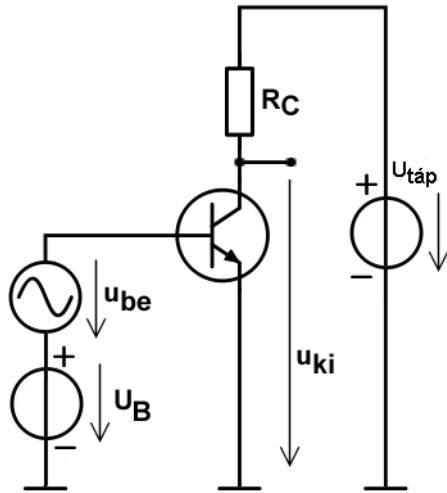

19. CE model

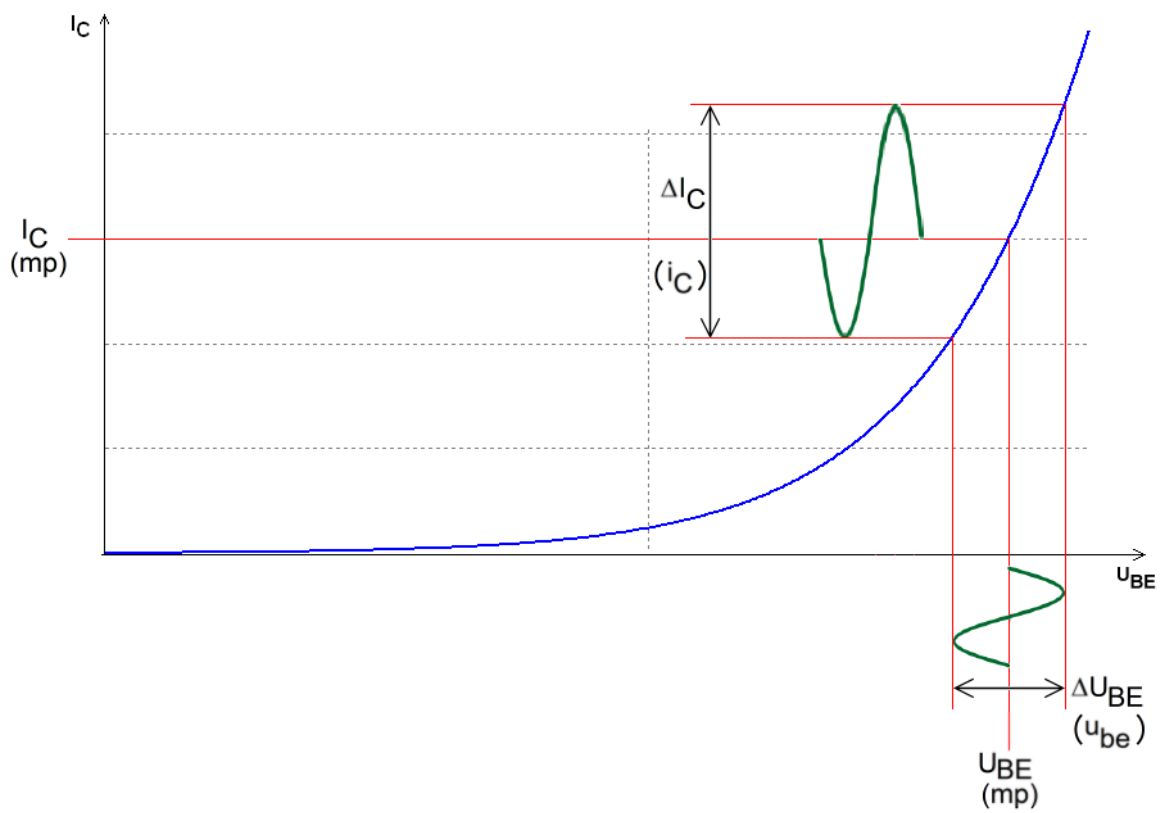

20.

Definition of gains (amplifications) for any amplifier:

$$A_V = \frac{v_{out}}{v_{in}}; \quad A_I = \frac{i_{out}}{i_{in}}; \quad A_P = \frac{P_{out}}{P_{in}}$$

Note that the **definition** is a formula that can be used to measure the quantity or to derive the actual formula for the given circuit.

We are going to find AV gain for the "*small signal approximation*". This means that the AC input signal ( $v_{in}$ ) is much smaller than the  $V_{BE}$  DC bias voltage. Thus the  $v_{in}$  projected onto the input or transfer characteristic curves will occupy only a short section, which will be treated as almost linear. See figure 20.

This way the connection between  $v_{in}$  and  $i_C$  can be given by the slope of the characteristic curve at the operating point.

The slope (also called transfer conductance, or transconductance in short) is defined generally as

$$g_{21} = \frac{\Delta I_{out}}{\Delta U_{in}} = \frac{i_{out}}{u_{in}}$$

Note: it's denoted by  $g$  as it is a conductance and thus measured in S (siemens). In Hungarian it is  $g_m$  (as slope is *meredekség*) also sometimes used in international literature (where  $m$  stands for *mutual*) In German its symbol is  $S$ . The lower case  $g$  shows that it is a ratio of changes, ie. a dynamic quantity.

This formula for  $g_{21}$  is universal, it can be applied to any device which has an input voltage - output current characteristic (such as other types of transistors or tubes).

In a bipolar CE amplifier this leads to:

$$g_{21} = \frac{\Delta I_C}{\Delta V_{BE}} = \frac{i_C}{u_{BE}}$$

Knowing the characteristic curve, we can find the transconductance at any operating point. It is the slope of the tangent line at the operating point, or in other words, the differential of the function at the operating point.

$$g_{21} = \frac{dI_C}{dV_{BE}} = \frac{d(I_{C0} e^{\frac{V_{BE}}{V_T}})}{dV_{BE}} = \frac{1}{V_T} I_{C0} e^{\frac{V_{BE}}{V_T}} = \frac{I_C}{V_T} \quad \left[ \frac{A}{V} = S \right]$$

where  $V_T=26mV$  (thermal voltage) at around 300K. körül) hányadosával. Result of  $g_{21}$  is usually in millisiemens.

Knowing  $g_{21}$  and the input signal we can get  $i_C$ , from which, knowing  $R_C$  we get the output voltage (first approximation).

The collector potential generally:

$$V_C = V_{\text{supply}} - V_{RC} = V_{\text{supply}} - I_C R_C$$

Here  $I_C$  has both a DC and an AC component. Now we only want to know the AC component (denoted by  $i_C$ ), so the DC components ( $V_{\text{supply}}$  and  $I_C$ ) disappear (but the negative sign stays):


$$v_{\text{out}} = v_C = -u_{RC} = -i_C \cdot R_C$$

Knowing that the  $v_{\text{in}} = v_{BE}$  in this circuit, take the formula for gain and substitute  $g_{21}$  into it:

$$A_V = \frac{v_{\text{out}}}{v_{\text{in}}} = \frac{-i_C R_C}{v_{\text{in}}} = -\frac{i_C}{v_{\text{in}}} R_C = -\frac{i_C}{v_{BE}} R_C = -g_{21} \cdot R_C$$

Note: This formula, by the way, is a generally true one for similar circuits (if you substitute  $r_{\text{out}}$  for  $R_C$ ). Ie. it is true for JFET and MOSFET and tube amplifiers as well in configurations similar to common emitter. It's the actual end formula for  $g_{21}$  that will differ.

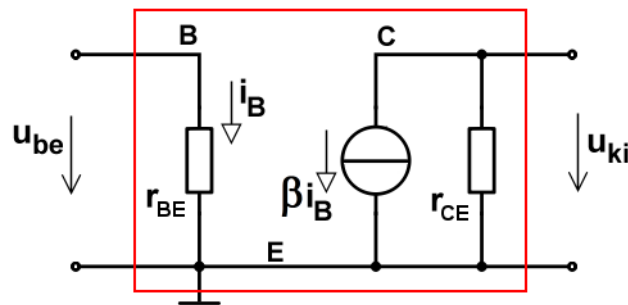A more accurate model of the amplifier follows, leading to a more accurate formula.



## 21. AC small signal model of transistor

The lower case  $r$  values are dynamic resistances, ie. ratios of change of voltage and change of current, or in other words, AC parameters.

This model is only true as long as the circuit gets an adequate dc power supply. But that is not shown here, as it is an AC model. We get this by using method of superposition. First turn off the AC sources and calculate all the DC voltages and currents (get the operating point). Then you can turn off the DC supply and turn on the AC input (the signal to be amplified) and calculate the AC values. (The order of these operations matters, as the AC parameters are dependent on the DC operating point.)

The input can be modeled by an impedance, for now simplified as a real resistance. This is modeled by  $r_{BE}$  - it is the input dynamic resistance of the transistor, ie change of  $V_{BE}$  over change of  $I_B$ . This determines the amplifier's input resistance.

As the  $V_{BE}$ - $I_B$  characteristic is again coming from the known diode equation, the result will be similar to the derivation of  $g_{21}$ .

$$r_{BE} = \frac{dV_{BE}}{dI_B} = \frac{1}{\frac{dI_B}{dV_{BE}}} = \frac{1}{\frac{dI_{B0} (e^{\frac{V_{BE}}{V_T}} - 1)}{dV_{BE}}} = \frac{V_T}{I_B}$$

The output contains a controlled (AC) current generator and an output dynamic resistance (Norton-model). The generator creates beta times the input current.

The output resistance is  $r_{CE}$ , already met when discussing the current generator circuit.

It is defined as

$$r_{CE} = \frac{dV_{CE}}{dI_C}$$

Normally it should be several ten or hundred k $\Omega$  minimum (in the saturated part of the curve!). It is greater, if  $I_C$  is smaller.

You can find h-parameters in many books and datasheet. These are practically equivalent to the notations here as follows:


$$\begin{aligned} h_{11e} &= r_{BE} \\ h_{21e} &= h_{FE} = \beta^1 \\ \frac{1}{h_{22e}} &= r_{CE} \end{aligned}$$

(Note that h-parameters have conditions for their measurement/definition, but we are not going to discuss that here.)

---

<sup>1</sup> Theoretically the DC value of beta is capital B, the small signal AC value of beta is lowercase  $\beta$  (defined as  $\beta = \frac{dI_C}{dI_B}$ ). The difference is not important now and the wide range of literature also differs greatly in usage and correctness. (I.e. h-parameters, indicated by the lowercase, should be AC as well, but still h21 is used for DC beta as well usually). We shall treat B and  $\beta$  as equal here.

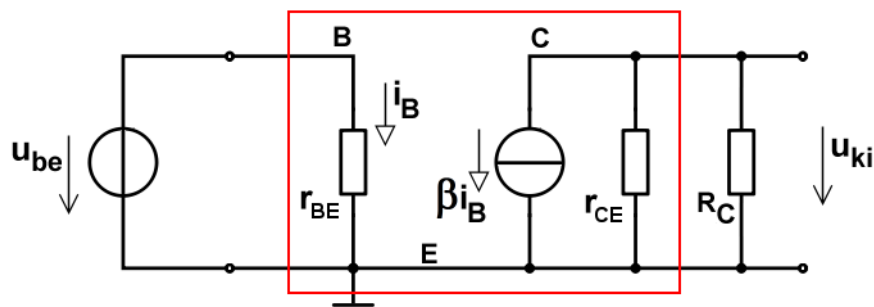Let's put  $R_C$  into our AC model now. Using superposition, deactivating the DC power supply, it becomes a short circuit to the ground (being a voltage source with zero internal resistance). Thus all resistors that are connected to the power supply, are connected to ground in AC. Thus  $R_C$  is here connected between collector and ground in AC, thus parallel with  $r_{CE}$ .



22. Unloaded amplifier AC model (no  $R_L$ )

$$i_B = \frac{V_{in}}{r_{BE}}$$

$$i_C = \beta \cdot i_B = \beta \frac{V_{in}}{r_{BE}}$$

2

$$u_{out} = -i_C \cdot (r_{CE} \parallel R_C) = \beta \frac{V_{in}}{r_{BE}} (r_{CE} \parallel R_C)$$

$$A_v = \frac{v_{out}}{V_{in}} = -\frac{\beta}{r_{BE}} (r_{CE} \parallel R_C)$$

This, at first sight, looks different from what we got earlier. (Unfortunately, many books stop here and give this as result and thus the student will not understand why the circuit is independent of beta).

But if we substitute the formula for  $r_{BE}$ :

$$r_{BE} = \frac{V_T}{I_B} = \frac{V_T \beta}{I_C}$$

$$A_v = -\frac{\beta}{r_{BE}} (r_{CE} \parallel R_C) = -\frac{\beta I_B}{V_T} (r_{CE} \parallel R_C) = -\frac{I_C}{V_T} (r_{CE} \parallel R_C) = -g_{21} (r_{CE} \parallel R_C)$$


we get a result that is familiar, only now extended by  $r_{CE}$ . In practice,  $r_{CE}$  is usually much greater than  $R_C$ , and thus can be neglected, getting back the earlier formula.

This way we can see that the gain does not depend on beta. The value of  $g_{21}$  is dependent on  $I_C$ . In reality the amplifier is based on the current generator (so as to get stable  $I_C$  for a stable gain) and thus we have an  $R_E$  which sets up  $I_C$  such that  $B$  practically doesn't affect it. Thus the gain is relatively stable.

<sup>2</sup> Remember: I'll be using the "parallel" symbol for calculating parallel net resistance. In Hungarian books it is often denoted by an  $\times$ , but that can be mistaken for multiplication or for cross product.


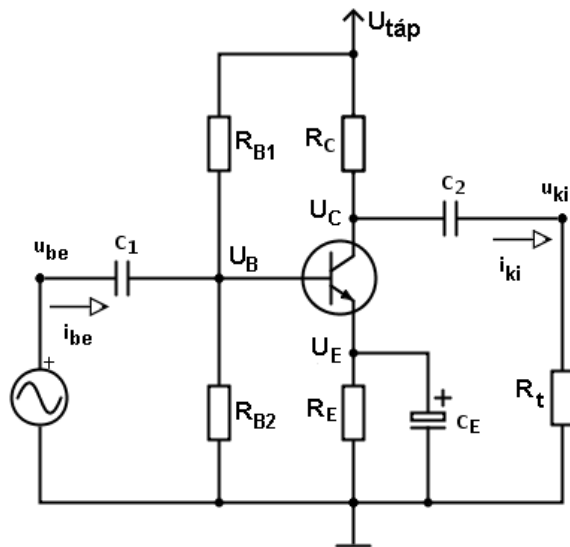
## Common emitter amplifier with one power supply



### 23. CE amplifier with AC coupling ( $R_t = R_{Load}$ )

We can see that this circuit is based on the current generator. As mentioned, the gain is dependent on  $I_C$ , therefore we want to keep  $I_C$  constant (in DC only, of course). Also,  $V_C$  determines the max output voltage swing (range), which is also important.  $V_C$  of course also depends on  $I_C$ .


The capacitors  $C_1$  and  $C_2$  disconnect the input and output in DC. This is required when the two sides have different DC voltage. Eg. in the laboratory, the input is gained from a function generator which has a DC voltage of 0V and very low output resistance; thus connecting it without  $C_1$  would make  $V_B=0$  as well.

The output capacitors makes  $I_C$  independent of  $R_L$  and is also important if the load circuitry needs different DC voltage. (In reality we often have several amps connected).

The emitter capacitor ( $C_E$ ) has another role. If it is not present, then  $R_E$  will create a negative feedback - it tries to keep  $I_C$  constant. That means it suppresses the AC component  $i_c$ , therefore it greatly decreases the gain. But we can't remove  $R_E$ , because it sets up the DC  $I_C$  current and stabilizes it. Therefore we put in  $C_E$ , which short circuits  $R_E$  only for purposes of AC signal. Therefore the earlier AC model we presented is still true, if the impedance of  $C_E$  is relatively small at the frequency of the input signal. This also means that at lower frequencies, the impedance of  $C_E$  is not low enough and thus some negative feedback still occurs. Thus  $C_E$  greatly determines the lower limit frequency.  $C_1$  and  $C_2$  also affect it, but  $C_E$  has the greatest effect.


For now, suppose that in operating frequency range all three capacitors can be considered short circuits (zero ohm).

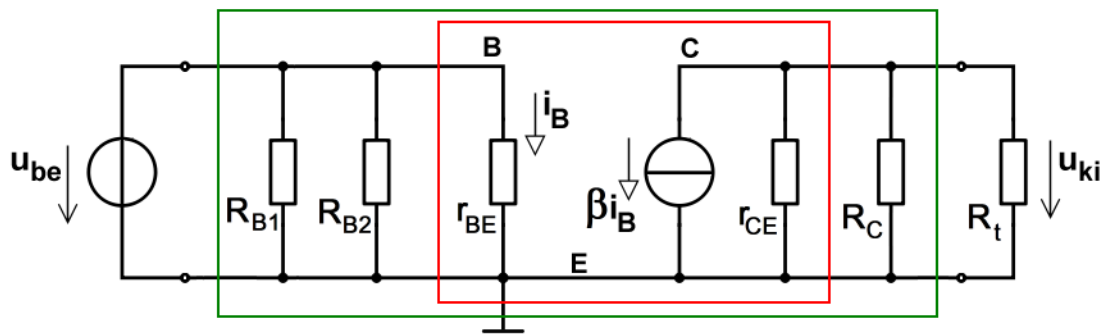Again, using superposition we find that  $R_{B1}$  and  $R_{B2}$  are both connected between base and ground and so actually in parallel in AC. We can now draw the full AC model:



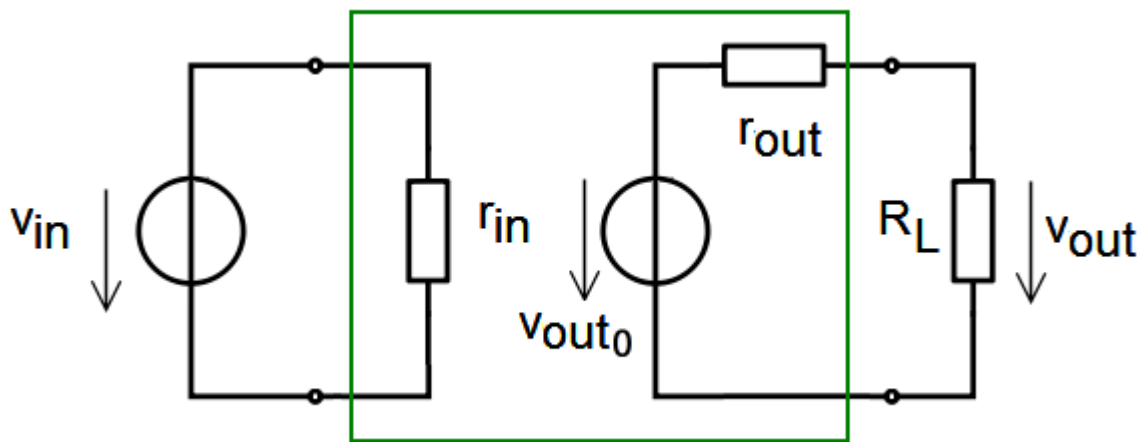24. AC small signal model of CE amplifier. Red: transistor model, green: amplifier circuit model

Let's take a look at a general model of any amplifier:



25. simplified model of a general amplifier

The amplifier can be modeled by a resistor on the input and a controlled generator at the output. Here I have drawn a Thevenin-model, as it is more well known probably, and is more useful in measurements. But remember that the transistor's model is actually a Norton-model (because of  $I_C = \beta I_B$ ). Also remember the two models can be changed into each other, so we can use both here.)

Let's find out these parameters for our CE amplifier:

$$r_{in} = R_{B1} \parallel R_{B2} \parallel r_{BE}$$

$$r_{out} = r_{CE} \parallel R_C$$

$$A_v = -g_m (r_{CE} \parallel R_C \parallel R_L) = -g_m (r_{out} \parallel R_t)$$

$$A_v \approx -g_m (R_C \parallel R_t), \text{ if } R_C \ll r_{CE}$$

$$A_v \approx -g_m R_C, \text{ if } R_C \ll r_{CE} \text{ and } R_L = \infty$$

So  $r_{CE}$  and  $R_C$  make up the output resistance. Don't forget that the load ( $R_L$ ) is not part of the amplifier and thus not part of the output resistance. If  $R_L$  is not present or very large, then approximate  $R_L = \infty$  which simplifies to the already known formula then.

Current gain is only present if there is a finite load:


$$A_I = \frac{i_{out}}{i_{in}} = \frac{\frac{v_{out}}{R_L}}{\frac{v_{in}}{r_{in}}} = \frac{v_{out}}{v_{in}} \cdot \frac{r_{in}}{R_L} = A_V \frac{r_{in}}{R_L}$$

Notice that this formula is independent of the actual circuit and so can be used generally for any amplifier where our model of 25 is true.

Power gain:

$$A_P = \frac{p_{out}}{p_{in}} = \frac{v_{out} \cdot i_{out}}{v_{in} \cdot i_{in}} = A_V \cdot A_I$$
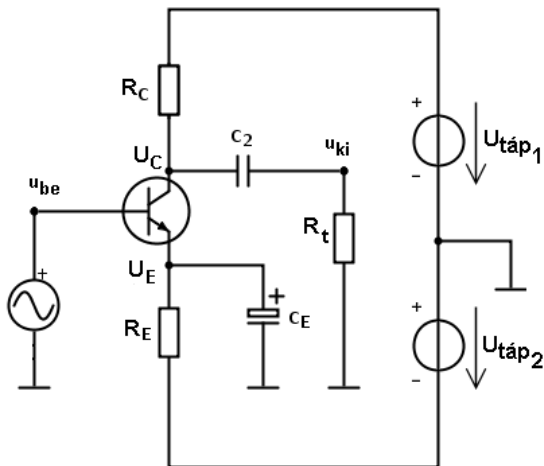
### *CE amplifier with double power supply*



26.

The CE amp can also be made with two power supplies. This removes the need for the base resistors. Here we supposed the input generator has DC voltage of zero, thus can be directly connected. Otherwise  $C_1$  capacitor would still be needed! In such a case the transistor's base has to be connected to the ground via a large resistor, to give it the zero volt operating point.

In this case the calculations in DC are similar as the double supplied current generators. AC calculations are similar to the single supplied amp, just  $R_{B1}$  and  $R_{B2}$  are not present in the equation (except if  $R_{B2}$  is connected because of using  $C_1$ ).

### ***Exercise: CE amplifier***

#### Parameters:

supply:  $V_0=20V$  ;

$R_{B1}=169k\Omega$  ;  $R_{B2}=33,2k\Omega$  ;  $R_C=5,1k\Omega$  ;  $R_E=2,21k\Omega$  ;  $R_L=7,15k\Omega$  ;

$C_E$  ;  $C_1$  ;  $C_2$  : very large;

$B=400$

$$V_B \approx V_0 \frac{R_{B2}}{R_{B1} + R_{B2}} = 3,28V$$

$$V_E = V_B - 0,7V = 2,58V$$

$$I_E = \frac{V_E}{R_E} = \frac{2,58V}{2210\Omega} = 1,17mA$$

$$I_C \approx I_E = 1,17mA$$

$$I_B = \frac{I_C}{B} = \frac{1,17mA}{400} = 2,92\mu A$$

$$V_C = V_0 - I_C R_C = 20V - 1,17mA \cdot 7,15k\Omega = 11,64V$$

$$r_B = \frac{V_T}{I_B} = \frac{26mV}{2,92\mu A} = 8,9k\Omega$$

$$r_{in} = r_B \parallel R_{B1} \parallel R_{B2} = 6,74k\Omega$$

$$r_{out} = R_C \parallel r_{CE} \approx R_C = 7,15k\Omega$$

$$g_{21} = \frac{I_C}{V_T} = \frac{1,17mA}{26mV} = 45mS$$

$$A_v = -g_{21}(r_{out} \parallel R_L) = -161$$

$$A_v (dB) = 20 \lg |A_v| = 44dB$$

$$A_I = A_v \frac{r_{in}}{R_L} = 152$$

Check for the validity of the starting supposition. (Note: checking for  $I_1$  or  $I_2$  are equally good.)

$$I_2 = \frac{V_B}{R_{B2}} = \frac{3,28V}{33,2k\Omega} \approx 100\mu A$$

$$I_B = \frac{I_C}{B} = \frac{1,17mA}{400} \approx 3\mu A$$

$$I_2 \geq 10 \cdot I_B$$

This means our supposition is acceptable (if not very good).

### ***Maximum output voltage, maximum gain***

The actual potential (ie at any time moment) of the collector can not exceed the positive power supply, or go below the emitter potential (because  $C_E$  keeps it constant). Thus the voltage swing (peaks) of the output are limited.

If the input signal times the gain would give larger signal than what the power supply, it will be cut off (made into a square wave).

Let's use a symmetric input signal (ie positive and negative peaks equal), such as a sine wave. Let's look at an unloaded circuit for simplicity.

For maximum output voltage peaks, we have to put VC in middle of its range:

$$V_C \leftarrow \frac{V_{\text{supply}} + V_E + V_{C_{E\text{sat}}}}{2} \approx \frac{V_{\text{supply}} + V_E}{2}$$

In practice we don't exactly keep this, but generally try to put VC around this value (roughly half the power supply value).

When  $R_L$  is present, the collector potential can not reach  $V_{\text{supply}}$ . If eg.  $R_C = R_L$  and operating point is  $V_C = V_{\text{supply}}/2$  for simplicity, then  $C_2$  (output capacitor) charges up to  $V_{\text{supply}}/2$ . The rest of the voltage (also  $V_{\text{supply}}/2$ ) is divided between the resistors evenly and thus  $V_C$  can only go up to  $3/4 V_{\text{supply}}$ . But in any case, driving the circuit to maximum would often cause too much distortion so we won't use the full range probably.

To find the maximum theoretical gain, suppose  $R_L$  is infinite (not present) and maximum output voltage range. Take the simplified circuit of figure 19.

$$V_C = \frac{V_{\text{supply}}}{2}$$

$$I_C R_C = V_{\text{supply}} - V_C = \frac{V_{\text{supply}}}{2}$$

$$g_{21} = \frac{I_C}{V_T}$$


$$A_{V_{\text{max}}} = -g_{21} R_C = -\frac{I_C R_C}{V_T} = -\frac{V_{\text{supply}}}{2V_T}$$

We can see that with these conditions, values of  $I_C$  and  $R_C$  are not independent, and the max gain is dependent only on power supply.

Gain can be greater than this, by the way - if we don't use the max range condition for VC - for example if our input signal is very small, so its amplified value is still below the max output, then max range doesn't matter as much and we can have greater gain.

Increasing  $R_C$  increases output resistance, which can be problematic. Increasing  $I_C$  increases power dissipation.
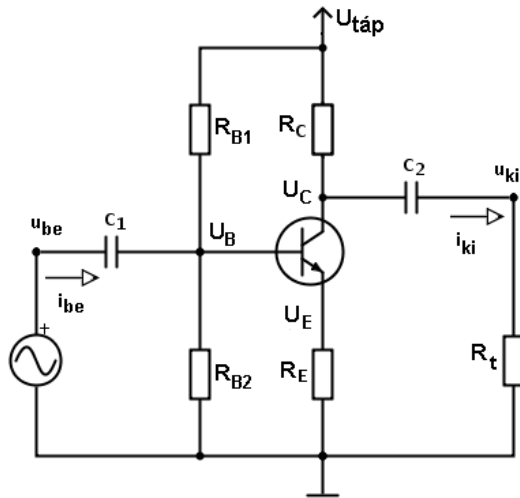
### 1.4.2. CE amp with emitter capacitor removed



27.

Taking CE out of the circuit, the emitter resistor's negative feedback effect will work in AC as well. Thus it will try to keep  $I_C$  from changing. But while very low-frequency changes are unwanted, we do want changes in the frequency of the input. So suppressing these means there will be very little useful AC signal on the output, ie. the gain is suppressed as well.

We can make an estimation on the voltage gain.

Now the input signal  $v_{in}$  fall only partly on BE junction, and partly on  $R_E$ . Remember the case of the diode+resistor. When the  $V_B$  is large enough compared to 0,7V, the majority of the change of voltage (ie.  $v_{in}$ ) will fall on  $R_E$ , and  $V_{BE}$  is approximately constant, ie.  $v_{BE}$  is very small, close to zero in AC. Thus in AC we can say  $v_E \approx v_{in}$ .

$$v_{in} = v_{BE} + v_E \approx v_E$$

$$i_E = \frac{v_E}{R_E} = \frac{v_{be}}{R_E}$$

$$i_C \approx i_E$$

$$v_{out} = -i_C R_C$$

$$A_v = \frac{v_{out}}{v_{in}} \approx \frac{-i_C R_C}{v_{in}} = \frac{-\frac{v_{in}}{R_E} R_C}{v_{in}} = -\frac{R_C}{R_E}$$

if loaded:

$$A_v = -\frac{R_C \parallel R_L}{R_E}$$

This is much smaller than the gain when  $C_E$  is present. (As the expression "negative feedback" should imply.)

This formula is only true as long as the initial assumption is true, that  $v_{BE}$  is small. If  $R_E$  is very small, for example, this will not hold true. The resulting gain can not be greater than that of the original circuit. So choosing for example  $R_C=5k\Omega$  and  $R_E=5\Omega$  would not make a thousand times gain.

The input resistance also changes. At first sight, we may say that  $R_E$  parallel to  $R_L$  is added to  $r_{BE}$ , but closer inspection tells us otherwise.

$$r_{in} = R_{B1} \parallel R_{B2} \parallel r'_{in}$$

$$r'_{in} = \frac{v_{in}}{i_B}$$


$$v_{in} = v_{BE} + v_E$$

$$r'_{in} = \frac{v_{BE} + v_E}{i_B} = \frac{v_{BE}}{i_B} + \frac{v_E}{i_B} = r_{BE} + \frac{v_E \beta}{i_C} = r_{BE} + \beta R_E$$

$$r_{in} = R_{B1} \parallel R_{B2} \parallel (r_{BE} + \beta R_E)$$

Because  $R_E$  has beta times the current compared to the input where we look at the resistance, the  $R$  is also seen as beta times greater. (Strictly speaking  $B+1$  times, but the difference is negligible if  $B$  is large enough.)
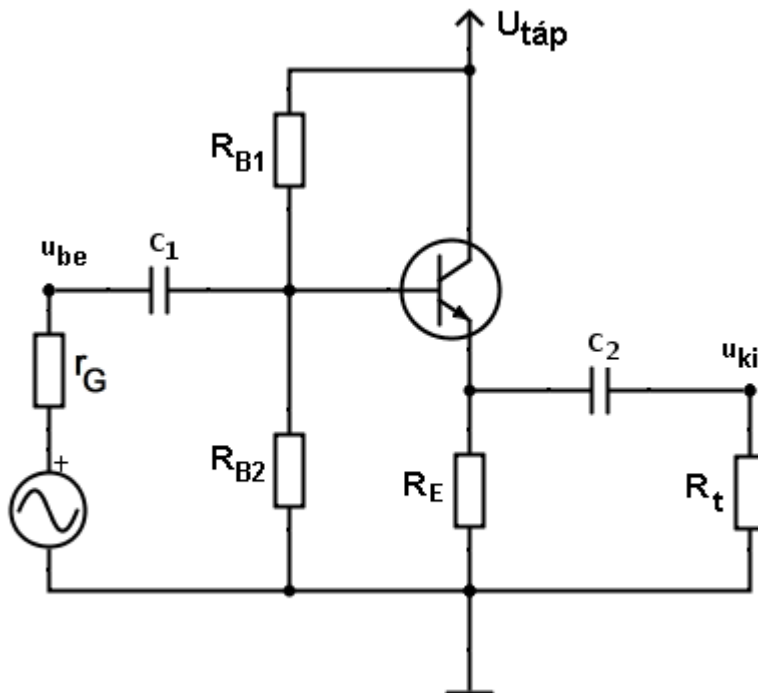
### 1.4.3. Common Collector amplifier (CC)



#### 28. CC amplifier

This amplifier has less than one voltage gain. It is used as an end stage amplifier to connect to low impedance loads. Connecting those to the high output resistance CE amp would lead to low power. The CC has high input resistance and low output resistance, thus makes it possible to connect to low impedance loads and have high power on the output. (Think about, for example, loudspeakers of 4 or 8 or 16 etc ohms of impedance...)

Voltage gain:

$$g_{21} = \frac{i_C}{u_{BE}} \Rightarrow i_C = g_{21} u_{BE}$$

$$v_{out} = v_E = i_E (R_E \parallel R_L) \approx i_C (R_E \parallel R_L) = g_{21} v_{BE} (R_E \parallel R_L)$$

$$v_{in} = v_{BE} + v_E = v_{BE} + g_{21} v_{BE} (R_E \parallel R_L) = v_{BE} (1 + g_{21} (R_E \parallel R_L))$$

$$AV = \frac{v_{out}}{v_{in}} = \frac{g_{21} v_{BE} (R_E \parallel R_L)}{v_{BE} (1 + g_{21} (R_E \parallel R_L))} = \frac{g_{21} (R_E \parallel R_L)}{1 + g_{21} (R_E \parallel R_L)}$$

If eg.  $I_C=1\text{mA}$  and  $R_E=5\text{k}\Omega$ , the unloaded gain is  $A_V=0,995$ .

If a load of  $R_L=26\Omega$  is used,  $A_V=0,5$ . (Similar values to 0,5 occur when load is similar to the output resistance, ie. we have power matching.)

The input impedance is similar to the CE without  $C_E$ .

$$r_{in} = R_1 \parallel R_2 \parallel (r_{BE} + \beta (R_E \parallel R_L))$$



For output resistance, we invert our previous logic. If the higher current output resistors seem beta times higher from the input, then the input resistors seem beta times smaller from the output. The transistor's BE junction's dynamic resistance is also different, as now we look at it from emitter side, so instead of  $r_{BE}$  we use  $r_{EB}$ .

$$r_{EB} = \frac{v_{BE}}{i_E} \approx \frac{v_{BE}}{i_C} = \frac{r_{BE}}{\beta} = \frac{1}{g_{21}}$$

$$r_{out} = R_E \parallel \left( r_{EB} + \frac{1}{\beta} (R_{B1} \parallel R_{B2} \parallel r_G) \right) = R_E \parallel \left( \frac{1}{\beta} (r_{BE} + R_{B1} \parallel R_{B2} \parallel r_G) \right)$$

Here the output resistance of the previous circuit or function generator,  $r_G$  is also seen. For a lab function generator  $r_G$  is usually  $50\Omega$ . It could also be a CE amplifier, with a few  $k\Omega$  output resistance. Divided by beta, it's still a small number. Therefore  $r_{out}$  is relatively small here.

Usually  $R_{B1}$  and  $R_{B2} \gg r_G$ , and  $R_E \gg (r_{EB} + r_G/\beta)$ , thus

$$r_{out} = R_E \parallel \left( r_{EB} + \frac{1}{\beta} (R_{B1} \parallel R_{B2} \parallel r_G) \right) \approx r_{EB} + \frac{r_G}{\beta}$$


If we take our previous CE circuits output resistance as  $r_G = 5k\Omega$  and  $\beta = 200$ :

$$r_{EB} = \frac{U_T}{I_C} = 26\Omega$$

$$r_{out} \approx r_{EB} + \frac{r_G}{\beta} = 26\Omega + 25\Omega = 51\Omega$$

### 1.5. Tricky questions


1.

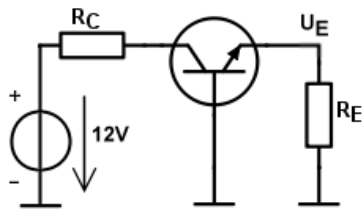

29.

Find  $I_E$ ,  $I_C$ ,  $V_C$  and  $V_E$ . ( $R_C=R_E=1k\Omega$ )

2.

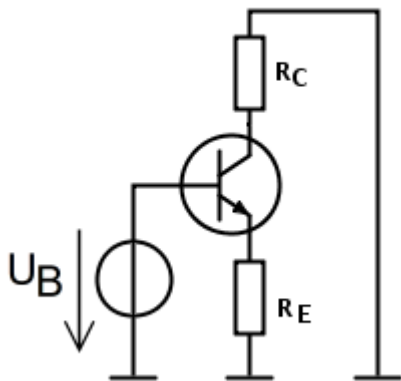

30.

Find  $I_C$  and  $I_E$  áramait (draw the arrows as well).  $V_B=5V$ ;  $R_E=R_C=1k\Omega$ .

3.

What happens if the Zener diode is used instead of  $R_{B2}$  in the CE amplifier?


## 1.6. Examples

### I.

Exercise: Design a BJT current generator for ohmic load!

Parameters:  $V_0=12V$  ;  $I_C=2mA$  ;  $B=200$  ;  $V_{CEsat}=0,2V$

Solution:

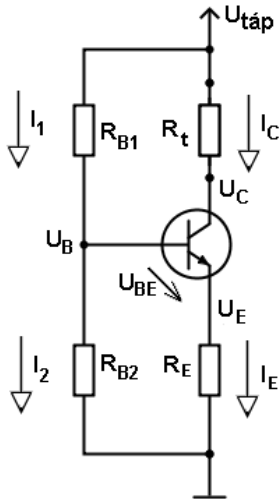

If  $R_{Lmax}$  is not given, we can choose  $V_E$  ourselves. A few volts is usually enough. Let's now choose  $V_E=2V$ .  $V_{BE}$  can be treated as  $0,7V$ . For  $B$  we used a minimum value listed in datasheet (taking a modern general low current transistor).

$$V_E = 2V$$

$$V_B = V_E + V_{BE} = 2,7V$$

$$I_E \approx I_C = 2mA$$

$$R_E = \frac{V_E}{I_E} = \frac{2V}{2mA} = 1k\Omega$$

In practice choosing  $I_1=10 \cdot I_B$  usually works.

$$I_1 = 10I_B = 100\mu A$$

$$I_2 = 9I_B = 90\mu A$$

$$R_{B1} = \frac{V_0 - V_B}{I_1} = \frac{12V - 2,7V}{100\mu A} = 93k\Omega$$

$$R_{B2} = \frac{V_B}{I_2} = \frac{2,7V}{90\mu A} = 30k\Omega$$

The load's maximum value can be calculated if we know  $V_{CEsat}$ . It is often not known precisely in advance. We can take its value to be a few hundred mV when  $I_C$  is a few mA. Let's use 0,2V now.


$$R_{L\_max} = \frac{V_0 - V_{CEsat} - V_E}{I_C} = \frac{12V - 0,2V - 2V}{2mA} = 4,9k\Omega$$

## II.

Exercise: Design a BJT current generator for ohmic load!

Parameters:  $U_0=5V$  ;  $I_C=100\mu A$  ;  $B=200$ ;  $V_{CEsat}=0,2V$ ;  $R_{Lmax}=30k\Omega$

Solution:

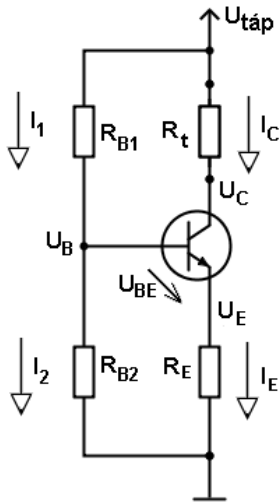

$R_{Lmax}$  is now given, thus  $V_E$  can not be freely chosen.

$$R_{Lmax} = \frac{V_0 - V_{CEsat} - V_E}{I_C}$$

$$V_E = V_0 - V_{CEsat} - I_C \cdot R_{Lmax} = 5V - 0,2V - 100\mu A \cdot 30k\Omega = 1,8V$$

(Note:  $R_{Lmax}$  can be treated as a minimum requirement, we can design for somewhat larger as well.)

$$V_B = V_E + V_{BE} = 2,5V$$

$$I_B = \frac{I_C}{B} = \frac{100\mu A}{200} = 0,5\mu A$$

$$I_E \approx 100\mu A$$

$$R_E = \frac{V_E}{I_E} = \frac{1,8V}{100\mu A} = 18k\Omega$$

$$I_1 = 10I_B = 5\mu\text{A}$$

$$I_2 = 9I_B = 4,5\mu\text{A}$$

$$R_{B1} = \frac{V_0 - V_B}{I_1} = \frac{5\text{V} - 2,5\text{V}}{5\mu\text{A}} = 500\text{k}\Omega$$

$$R_{B2} = \frac{V_B}{I_2} = \frac{2,5\text{V}}{4,5\mu\text{A}} = 555\text{k}\Omega$$

*Variation for base divider:*

When the base current is so small as here, we may choose greater  $I_1$  than the  $10I_B$ .

For example choose  $500I_B$ .

$$I_1 = 500I_B = 250\mu\text{A}$$

$$I_2 = 499I_B = 249,5\mu\text{A}$$

$$R_{B1} = \frac{V_0 - V_B}{I_1} = \frac{5\text{V} - 2,5\text{V}}{250\mu\text{A}} = 10\text{k}\Omega$$

$$R_{B2} = \frac{V_B}{I_2} = \frac{2,5\text{V}}{249,5\mu\text{A}} = 10,02\text{k}\Omega \approx 10\text{k}\Omega = \frac{2,5\text{V}}{250\mu\text{A}}$$


The result for  $R_{B2}$  is well within the normal tolerance of a  $10\text{k}\Omega$  resistor (because here we had 499 vs 500 difference instead of 9 vs 10 in the currents). Thus here we can safely say  $R_{B2}=10\text{k}\Omega$ . As the base potential was set up to be half power supply, we can just take two equal resistors of a few  $\text{k}\Omega$  and not even have to calculate much.

### III.

Exercise: Calculate all voltages and currents and  $R_{L_{max}}$ !

Parameters:  $V_0=15V$  ;  $B=200$ ;  $R_{B1}=100k\Omega$ ;  $R_{B2}=50k\Omega$ ;  $R_E=2,2k\Omega$ ;  $V_{CEsat}=0,2V$

Solution:

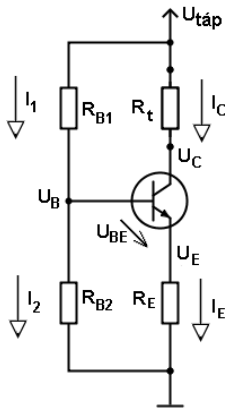

Here we can not use the rule  $I_1=10 \cdot I_B$ , as it is a design method, not a physical law. Also, even if we found out the value of  $I_B$ , we can't find  $I_C$  from saying  $I_C=BI_B$ , as value of  $B$  is very uncertain.

We estimate base potential:

Suppose:  $I_1 \gg I_B$ , so  $I_1 \approx I_2$

$$V_B = V_0 \frac{R_{B2}}{R_{B1} + R_{B2}} = 15V \cdot \frac{50k\Omega}{100k\Omega + 50k\Omega} = 5V$$

Let's use  $V_{BE}=0,7V$ .

$$V_E = V_B - 0,7V = 4,3V$$

$$I_E = \frac{V_E}{R_E} = \frac{4,3V}{2,2k\Omega} = 1,95mA$$

$$B > 100 \rightarrow I_C = I_E = 1,95mA$$

$$R_{L_{max}} = \frac{V_0 - V_{CEsat} - V_E}{I_C} = \frac{15V - 0,2V - 4,3V}{1,95mA} = 5,37k\Omega^3$$

Check our initial estimation:

$$I_2 = \frac{V_B}{R_{B2}} = \frac{5V}{50k\Omega} = 0,1mA$$

$$I_B = \frac{I_C}{B} = \frac{1,95mA}{200} \approx 0,01mA$$

$$I_2 \geq 10 \cdot I_B$$

Thus our estimation is not bad.


<sup>3</sup> Before you say that 5,38k is the correct value: the previous values were written down in rounded form, but saved in more precise form in the calculator's memory..

#### IV.

Exercise: Design a BJT current generator with PNP transistor for driving a white LED!

Parameters:  $I_{LED}=400\text{mA}$  ;  $V_{LED}=3\text{V}$  ;  $B=200$  ;  $V_{CEsat}=0,2\text{V}$  ;  $V_{EB}(I_C=400\text{mA})=0,9\text{V}$

Solution:

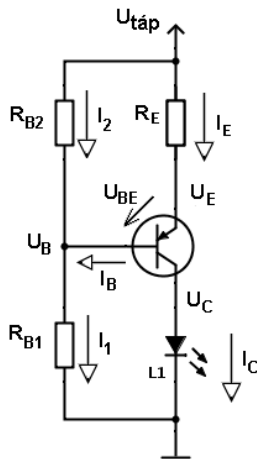

For PNP transistors, all voltage and current arrows are reversed. Therefore we usually connect them with emitter towards the supply. The forward bias needs emitter to be more positive than the base.

I chose a transistor where the  $V_{EB}$  is listed as  $0,9\text{V}$  for  $400\text{mA}$   $I_C$ . (The current is high, probably a bit high for this transistor, but should work.)

Here the power supply voltage is not specified, we have to choose it. Data sheet says  $V_{CEsat}$  is about  $0,2\text{V}$  at  $400\text{mA}$   $I_C$ . Let us design with safety margin, give  $V_{EC}=1\text{V}$  to get  $V_E=V_{LED}+V_{EC}=4\text{V}$ .

If we use the commonly found  $5\text{V}$  supply then we still have  $V_{RE}=1\text{V}$ , which is acceptable, thus the  $5\text{V}$  supply is also acceptable.

$$V_0 = 5V$$

$$V_{EB} = 0,9V$$

$$V_C = V_{LED} = 3V$$

$$V_{RE} = 1V$$

$$V_E = V_0 - V_{RE} = 4V$$

$$I_B = \frac{I_C}{\beta} = \frac{400mA}{200} = 2mA$$

$$I_E = I_C + I_B = 402mA \approx 400mA$$

$$R_E = \frac{V_{RE}}{I_E} = \frac{2V}{400mA} = 5\Omega$$

$$V_B = V_E - V_{EB} = 3,1V$$

$$I_1 = I_2 + I_B$$

$$I_1 = 10I_B = 20mA$$

$$I_2 = 9I_B = 18mA$$

$$R_{B1} = \frac{V_B}{I_1} = \frac{3,1V}{20mA} = 155\Omega$$

$$R_{B2} = \frac{V_0 - V_B}{I_2} = \frac{1,9V}{18mA} = 105,5\Omega$$

When current is more than about 100mA, it is advisable to calculate with powers as well.

$$P_{LED} = V_{LED} \cdot I_C = 3V \cdot 400mA = 1,2W$$

$$P_{RE} = V_{RE} \cdot I_E = 1V \cdot 400mA = 400mW$$

$$P_{transistor} \approx V_{EC} \cdot I_C = 1V \cdot 400mA = 400mW$$

This means we should use a resistor designed for minimum 0,5W power as RE. The transistor datasheet mentions 700mW max power, so it is good, but probably requires a heat sink. The LED parameters are from its datasheet's default values, so should be right as well, but cooling is required here.

I chose (somewhat randomly) a 12A02CH transistor and a Cree XLamp XP-G LED for this exercise.




V.

Exercise: Calculate parameters of this CE amp!

Parameters:  $V_1=10V$  ;  $V_2=5V$  ;  $R_C=2,49k\Omega$ ;  $R_E=2,15k\Omega$  ;  $R_L=5k\Omega$  ;  $C_E=100\mu F$  ;  $C_2=10\mu F$  ;  $B=400$

Solution:

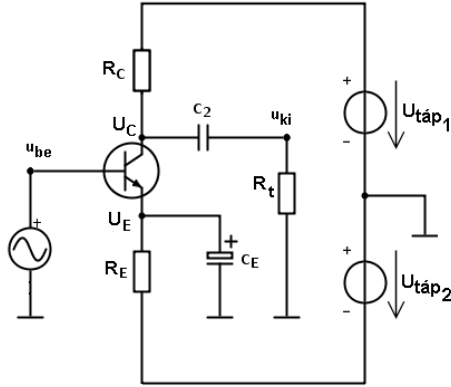

$$V_B = 0V$$

$$V_{BE} = 0,7V$$

$$V_E = V_B - V_{BE} = -0,7V$$

$$V_{RE} = V_E - (-V_{táp2}) = 4,3V$$

$$I_E = \frac{V_{RE}}{R_E} = \frac{4,3V}{2150\Omega} = 2mA$$

$$I_C \approx I_E = 2mA$$

$$I_B = \frac{I_C}{B} = 5\mu A$$

$$V_C = V_1 - I_C R_C = 10V - 2mA \cdot 2,49k\Omega = 5,02V \approx 5V$$

$$r_B = \frac{V_T}{I_B} = \frac{26mV}{5\mu A} = 5,2k\Omega$$

$$r_{in} = r_B = 5,2k\Omega$$

$$r_{out} \approx R_C = 2,49k\Omega$$

$$g_{21} = \frac{I_C}{V_T} = \frac{2mA}{26mV} = 77mS$$

$$A_V = -g_{21}(r_{out} \times R_L) = -g_m(R_C \times R_L) = -77mS \cdot \frac{2490 \cdot 5000}{2490 + 5000} \approx -128$$

$$a(dB) = 20 \lg |A_V| = 42dB$$

$$A_I = A_V \frac{r_{in}}{R_L} = -128 \cdot \frac{5200}{5000} = -133$$

